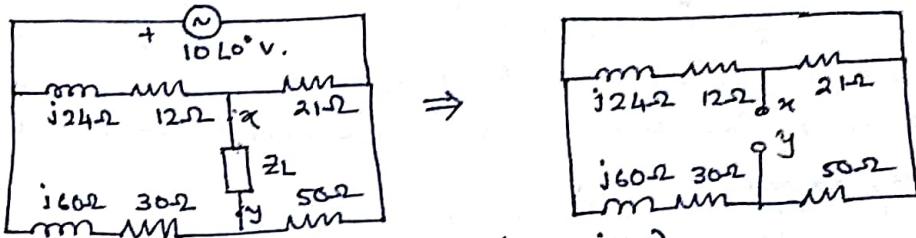


Maximum Power Transfer Theorem:

In the network find the value of Z_L so that the power transfer from the source is maximum. Also find P_{max} .



$$\begin{aligned} Z_{in} &= \frac{21(12+j24)}{21+12+j24} + \frac{50(30+j60)}{50+30+j60} \\ &= \frac{252+j504}{33+j24} + \frac{1500+j3000}{80+j60} \\ &= \frac{56.3 \cdot 4.16 L 63.43^\circ}{40-8 L 36^\circ} + \frac{3354.16 L 63.43^\circ}{100 L 36 \cdot 87^\circ} \\ &= (42.26 + j21.35) \Omega. \end{aligned}$$

As per max. power transfer theorem Z_L should be complex conjugate of Z_{in} .

$$\therefore Z_L = Z_{in}^* = (42.26 - j21.35) \Omega.$$

To Find $V_{o.c.}$

Let at x potential is V_x
at y potential is V_y .

$$V_x = \frac{12+j24}{12+j24+21} \times 10 L 0^\circ. \text{ (voltage division rule).}$$

$$= \frac{268 \cdot 33 L 63.43^\circ}{40-8 L 36^\circ} = 6.577 L 27.43^\circ V.$$


$$\text{Similarly } V_y = \frac{30+j60}{30+j60+50} \times 10 L 0^\circ = \frac{670.82 L 63.43^\circ}{80+j60} = 6.71 L 26.56^\circ V.$$

$$V_{o.c.} = V_x - V_y$$

$$\approx 0.1657 L 170^\circ V.$$

$$\therefore P_{max} = \frac{V_{oc}^2}{4RL} = \frac{0.1657^2}{4 \times 42.16} = 0.1624 mW.$$

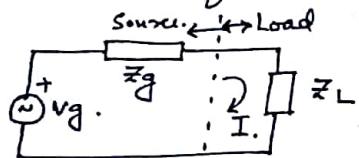④ Maximum Power Transfer Theorem in A.C Circuit:
 In a linear network having energy sources and impedances, maximum amount of power is transferred from source to load impedance if the load impedance is complex conjugate of the total impedance of the network. If the source impedance is $(R_g + jx_g) \Omega$, to have maximum power transfer, the load impedance must be $(R_L - jx_L) \Omega$.



$$\text{obviously, } I = \frac{V_g}{Z_g + Z_L} = \frac{V_g}{(R_g + R_L) + j(x_g + x_L)}$$

$$\therefore \text{Power (real power)} P_L = I^2 R_L.$$

$$= \frac{V_g^2}{(R_g + R_L)^2 + (x_g + x_L)^2} \times R_L.$$

$$\text{condition for maximum power flow } \frac{dP_L}{dx_L} = 0 \quad (\text{Hence})$$

$$\begin{aligned} \frac{dP_L}{dx_L} &= \frac{d}{dx_L} \left[\frac{V_g^2 R_L}{(R_g + R_L)^2 + (x_g + x_L)^2} \right] \\ &= \frac{-V_g^2 R_L \cancel{2(x_g + x_L)}}{[(R_g + R_L)^2 + (x_g + x_L)^2]^2} \end{aligned}$$

$$\text{Setting } \frac{dP_L}{dx_L} = 0, \quad x_g = -x_L.$$

$$\text{Substituting } x_g = -x_L,$$

$$* P_L = \frac{V_g^2 R_L}{(R_g + R_L)^2} = \frac{V_g^2}{4R_g} \left[1 - \left(\frac{R_g - R_L}{R_g + R_L} \right)^2 \right].$$

It may be seen that P_L would attain maximum provided $R_g = R_L$. Thus maximum power transfer place in a.c n/w provided $R_g = R_L$ and $x_g = -x_L$ in other words $(R_g + jx_g) = (R_L - jx_L)$ i.e. $Z_g = Z_L^*$. This means load impedance is the complex conjugate of the source impedance.

$$P_{\max} = \frac{V_g^2}{4R_L}, \quad \eta = 50\%.$$

$$* \frac{dP_L}{dR_L} = 0, \quad \frac{dP_L}{dR_L} = \frac{V_g^2 (R_g + R_L)^2 - 2V_g^2 R_g (R_g + R_L)}{(R_g + R_L)^4} = 0$$

$$\text{or, } V_g^2 (R_g + R_L) - 2V_g^2 R_g = 0$$

$$\text{or, } R_g = R_L.$$

Statement
 If a
 in a Lin
 algebraic
 each so
 by their
 Explan
 in fig
 source

New
 by

H

A

SUPERPOSITION THEOREM


P. Nabanta Chatterjee
(EE Dept.)

Statement:

If a no. of voltage or current sources are acting simultaneously in a linear network, the resultant current in any branch is the algebraic sum of the currents that would be produced in it, when each source acts alone replacing all other independent sources by their internal resistances.

Explanation:

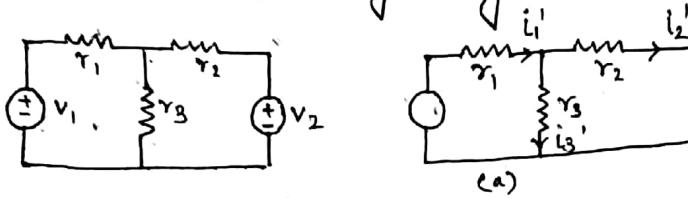In fig. to apply superposition theorem, let us first take the source V_1 alone replacing V_2 by short circuit. (a).



$$\text{Here, } i_1' = \frac{V_1}{\frac{r_2 r_3}{r_2 + r_3} + r_1}$$

$$i_2' = i_1' \frac{r_3}{r_2 + r_3} \quad \text{and} \quad i_3' = i_1' - i_2'$$

Next, removing V_1 by short circuit, let the circuit be energized by V_2 only.



$$\text{Here, } i_2'' = \frac{V_2}{\frac{r_1 r_3}{r_1 + r_3} + r_2} \quad \text{and} \quad i_1'' = i_2'' \frac{r_3}{r_1 + r_3}$$

$$\text{Also, } i_3'' = i_2'' - i_1''$$

As per superposition theorem

$$i_3 = i_3' + i_3''$$

$$i_2 = i_2' - i_2''$$

$$i_1 = i_1' - i_1''$$


It may be noted that during application of superposition the directions of currents calculated for each source should be taken care of.

Steps for Solving a Network Using the Principle of Superposition

- Step 1: Take only one independent source of voltage/current, deactivate the other independent voltage/current source, find I_1 for voltage sources, remove the source and short the respective circuit terminals and for current sources, just delete the source keeping the respective circuit open. Obtain branch currents.
- Step 2: Repeat the above step for each of the independent sources.
- Step 3: To determine the net branch current utilising Superposition Theorem, just add the currents obtained in Step 1 and Step 2 for each branch. If the currents obtained in Step 1 and Step 2 are in same direction, just add them; on the other hand, if the respective currents are directed opposite in each step, assume direction of the clockwise current to be +ve and the current obtained in the next step from the original current. The net current in each branch is then -ed.

Problems:

Find I in the circuit shown.

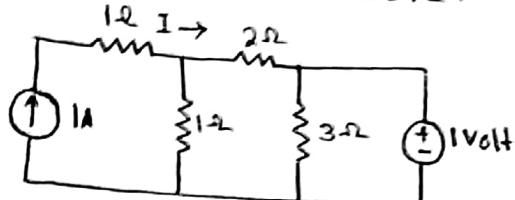


- Q1. Principle of superposition is applied by taking 1V source only at first.



$$I_s = \frac{1V}{[(1+2)||3]\Omega} = (1/1.5)A.$$

$$I_1 = I_s \cdot \frac{3}{3+2+1} = \frac{1}{1.5} \times \frac{3}{6} = \frac{1}{3}A. \quad [\text{by current division}]$$

Next, only current source is present.

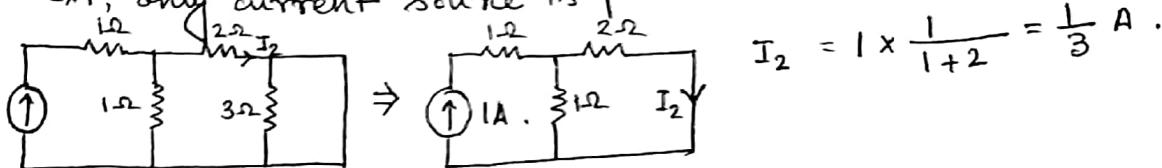


$$I_2 = 1 \times \frac{1}{1+2} = \frac{1}{3}A.$$

It may be observed that utilising the principle of superposition, the net response can be obtained when both the sources (1A and 1V) are present. The current through 2Ω resistor is obtained as.


$$I = (I_1 - I_2) = \frac{1}{3} - \frac{1}{3} = 0$$

[I_1 and I_2 being directed reverse]

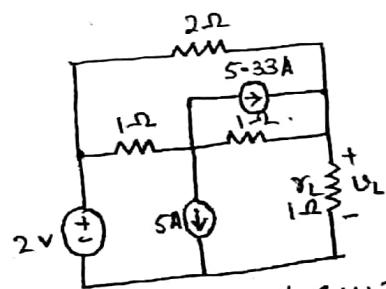- Q2. Find V_L in the circuit using superposition theorem.



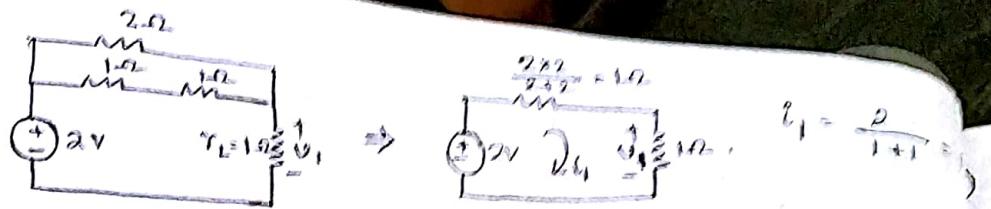
Let us first take 2V source deactivating the current sources.




$$\frac{2 \times 2}{2 + 2} = 1\Omega$$

$$i_1 = \frac{2}{1+1} = 1A$$
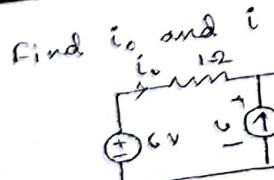
$$\therefore V_1 (\text{drop across } R_L \text{ due to } 2V) \\ = 1 \times 1 = 1V$$



Next Lower Current Source only

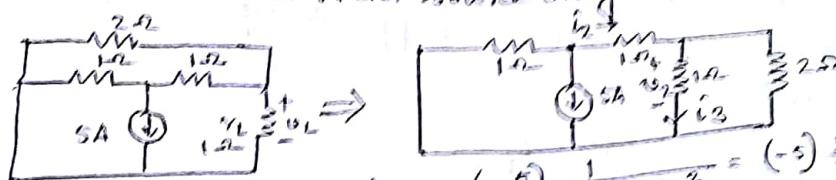


$$i_2 = (-5) \frac{1}{1+1+\frac{2}{3}} = (-5) \frac{2}{3} = -\frac{10}{3} A$$

$$\therefore i_3 = -\left(\frac{10}{3}\right) \times \frac{2}{2+1} = -\left(\frac{10}{3}\right) \frac{2}{3} = -\frac{20}{9} A.$$

$$\text{This gives } V_2 = -\frac{5}{4} \times 1 = -\frac{5}{4} V.$$

Next 5.33A source only

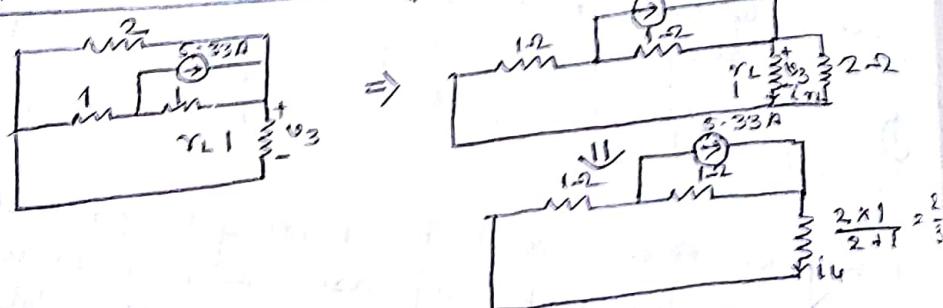

$$i_4 = 5.33 \times \frac{1}{2 + \frac{2}{3}} = 3 A.$$

$$\text{This gives } i_{RL} = 3 \frac{2}{2+1} = 2 A.$$

$$\therefore V_3 = 2 \times 1 = 2V.$$

By superposition,
 $V_L = V_1 + V_2 + V_3 = 1 + \left(-\frac{5}{4}\right) + 2 = \frac{7}{4} V = 1.75 V$

1A source




$$1 =$$

But $i_o'' =$
we find
i.e. i_o''


using

and

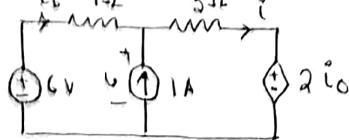Find i_0 and i from the circuit using Superposition Th.



Assume only 6V source to be active.

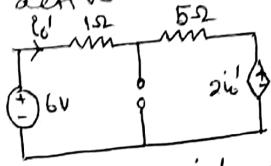


$$-6 + (1+5)i_0' + 2i_0' = 0$$

$$\text{or, } 8i_0' = 6 \therefore i_0' = \frac{3}{4} A$$

$$\therefore i_0' = i = \frac{3}{4} A$$

1A source active only

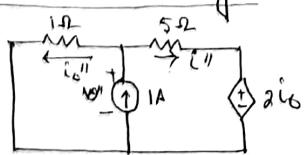

$$I = i_0'' + i''$$

$$= \frac{6''}{1} + \frac{6'' - 2i_0''}{5}$$

$$= 1.2i_0'' - 0.4i_0''$$

$$\text{But } i_0'' = \frac{6''}{1}$$

$$\text{we finally get, } I = 1.2i_0'' - 0.4i_0'' = 0.8i_0''$$

$$\text{i.e., } i_0'' = 1.25 A \text{ and } i'' = \frac{6'' - 2i_0''}{5}$$

$$= -i_0''/5 = -0.25 A$$


Using the principle of superposition,

$$i_0 = i_0' - i_0'' = \frac{3}{4} - 1.25 = -0.5 A$$

$$\text{and } i = i_0' + i'' = \frac{3}{4} - 0.25 = 0.5 A$$

Superposition (with A.C.):

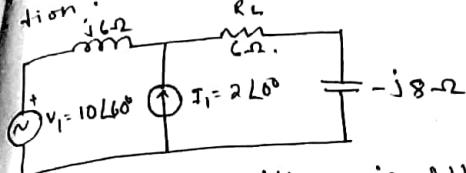Find the current in the resistor (R_L) using the principle of superposition.



Principle of superposition is applied in the given ckt. taking each source at a time.

$$I_1' = I \frac{j6}{j6+6+(-j8)} = \frac{2L0^\circ \times 6L90^\circ}{6-j2} = \frac{12M0^\circ}{6.32L-18.43^\circ} = 1.9L108.43^\circ A.$$


On the other hand, in next case.

$$I_1'' = \frac{V_1}{j6+6-j8} = \frac{10L60^\circ}{6-j2} = \frac{10L60^\circ}{6.32L-18.43^\circ}$$


$\therefore I$, the total current through R_L is $I = I_1' + I_1''$ (since both are directed in same dir.).

$$\begin{aligned} I &= 1.9L108.43^\circ + 1.58L78.43^\circ \\ &= -0.6 + j1.8 + 0.32 + j1.55 \\ &= (0.28 + j3.35) = 3.362L94.71^\circ A. \end{aligned}$$

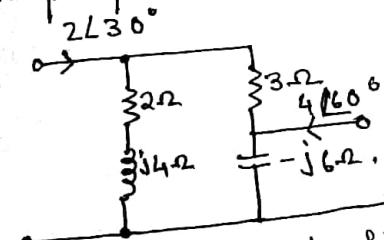D) Find the current in the $(-j6\Omega)$ capacitive reactance using superposition theorem in the circuit.




Let us apply it first to the fig.

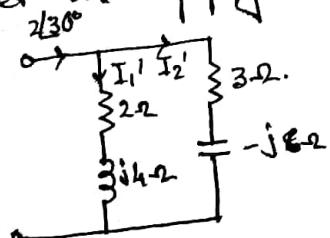

$$\begin{aligned} I_2' &= 2L30^\circ \frac{(2+j4)}{(2+j4)+(3-j8)} \\ &= \frac{8.944L93.44^\circ}{5-j2} = \frac{8.944L93.44^\circ}{5.385L-21.80^\circ} \\ &= 1.661L115.24A. \end{aligned}$$

Next it is applied to the next fig.

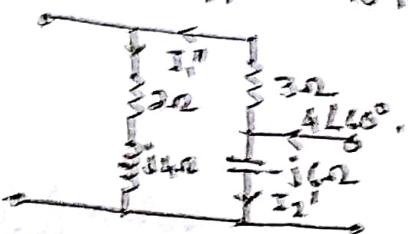

$$I_2'' = 4L60^\circ \frac{(3+2+j4)}{(3+2+j6)-j6} = \frac{4L60^\circ(5+j4)}{5-j2}$$
$$= \frac{4L60^\circ \times 6.4L38.66^\circ}{5-3.85L-21.80^\circ}$$
$$= 4.754 L120^\circ 46^\circ A.$$


Using the principle of superposition.

$$I_2 = I_2' + I_2'' = 1.661 L115.24 + 4.754 L120^\circ 46^\circ$$
$$= -0.7083 + j1.5 - 2.41 + j4.098$$
$$= -3.118 + j5.598 = 6.41 L119.117^\circ A.$$

Thus the current through the capacitor is

$$6.41 L119.117^\circ A.$$

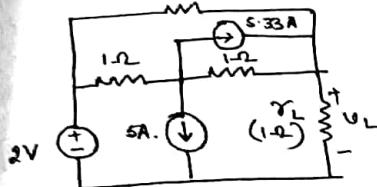
Find v_L in the circuit of Fig. using Superposition Theorem.




First only 2V source deactivating the ct. sources.

$$i_1 = \frac{2}{\frac{2 \times 2}{2+2} + 1} = 1 \text{ A.}$$

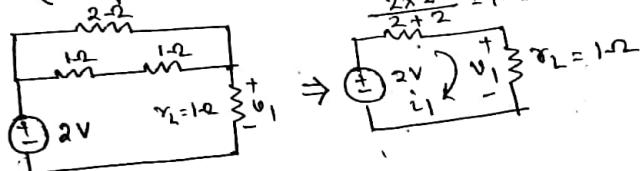$\therefore v_1$ (drop across r_L due to 2V source) $= 1 \times 1 = 1 \text{ V.}$



Next, lower current source only.

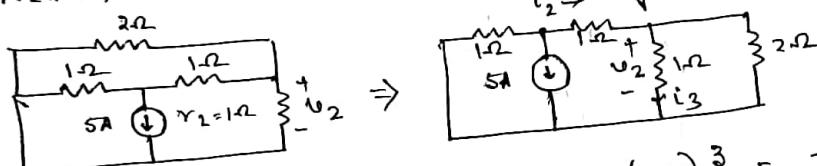


$$i_2 = (-5) \frac{1}{1 + 1 + 2/3} = (-5) \frac{3}{8} = -\frac{15}{8} \text{ A.}$$

$$i_3 = -\left(\frac{15}{8}\right) \cdot \frac{2}{1+2} = -\frac{5}{4} \text{ A.}$$

This gives $v_2 = -\frac{5}{4} \times 1 = -\frac{5}{4} \text{ V.}$

Next upper ct. source

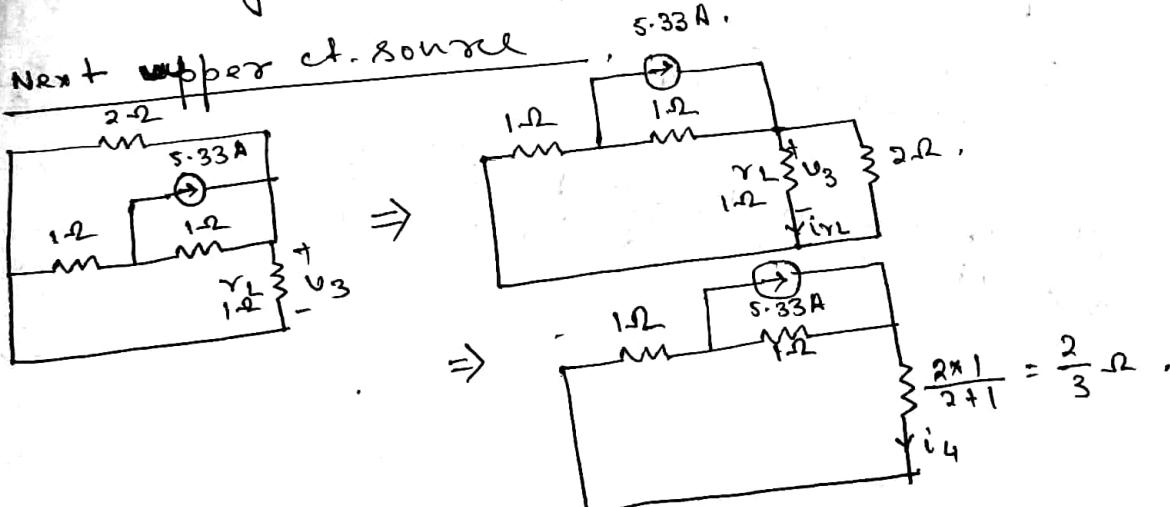



$$i_4 = 5.33 \cdot \frac{1}{\frac{2}{3} + 2} = 3 \text{ A.}$$

This gives. $i_{R_L} = 3 \cdot \frac{2}{2+1} = 2A$.


$$\therefore V_3 = 2 \times 1 = 2V.$$

$$\text{By superposition, } V_L = V_1 + V_2 + V_3 \\ = 1 + (-\frac{5}{4}) + 2 = \frac{7}{4}V \\ = 1.75V.$$

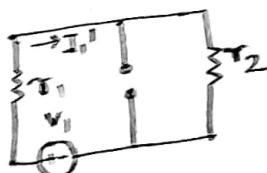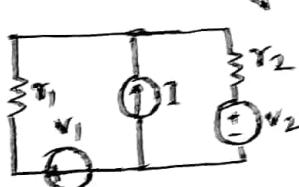
* Find current through R_1 , [$V_1 = 12V$, $R_1 = 4\Omega$, $I = 3A$, $R_2 = 2\Omega$]



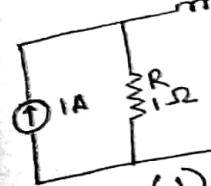
$$I' = \frac{V_1}{R_1 + R_2} = \frac{12}{4+2} = \frac{12}{6} A$$




Next only $V_2 \Rightarrow$

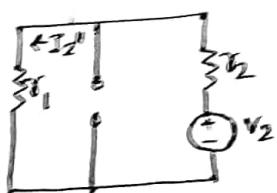
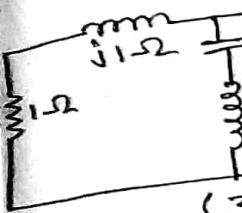
$$I'' = \frac{V_2}{R_1 + R_2} = \frac{24}{4+2} = \frac{24}{6} A$$



Next I only \Rightarrow


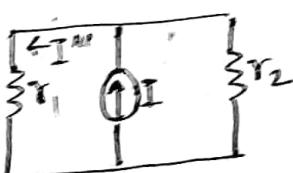


$$\text{Here } I''' = I \cdot \frac{R_2}{R_1 + R_2} = 3 \cdot \frac{2}{2+4} = 1A$$

Taking note that I'' and I''' are in reverse direction in comparison to I' , using the principle of superposition

$$I = I' - I'' - I''' \\ = 2 - 4 - 1 = -3A$$

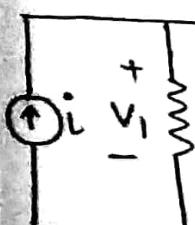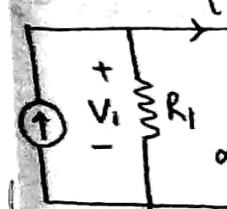The net current through R_1 will flow downward and its magnitude will be 3A.





Calculated by the
j.s.m


Therefore
voltage a
simultane

using the
voltage
 $C = 2F$

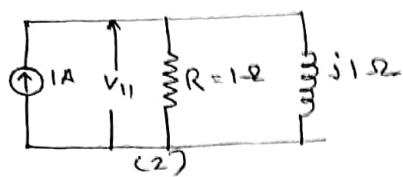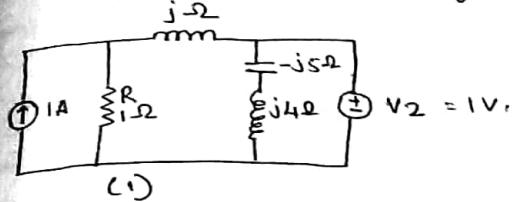Calculate Voltage V across the resistance R , in fig., by the principle of superposition.




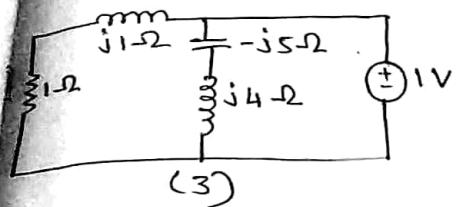
Making $V_2 = 0$ (shorted), $V_{11} = \frac{1}{1-j}$




Making $I_1 = 0$ (opened), $V_{12} = \frac{1}{1+j}$.

Therefore, by the superposition principle the voltage across R when both I_1 and V_2 are applied simultaneously, $V = V_{11} + V_{12} = 1$ volt.

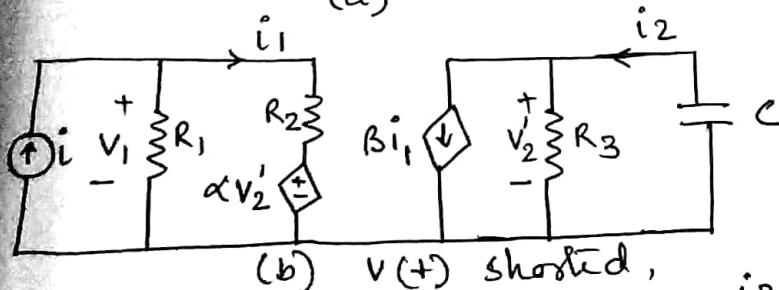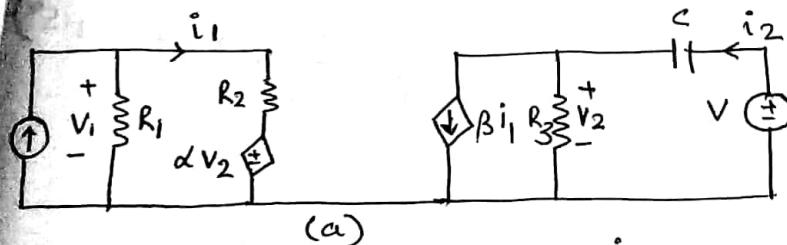directly, using the principle of superposition, calculate the voltage $V_2(+)$ in fig. Assume $R_1 = R_2 = 1\Omega$, $R_3 = 0.5\Omega$, $C = 2F$, $\beta = 2$, $\alpha = 1$, $i(+)$ = sin(+), $v(+)$ = t.



$V(+)$ shorted,

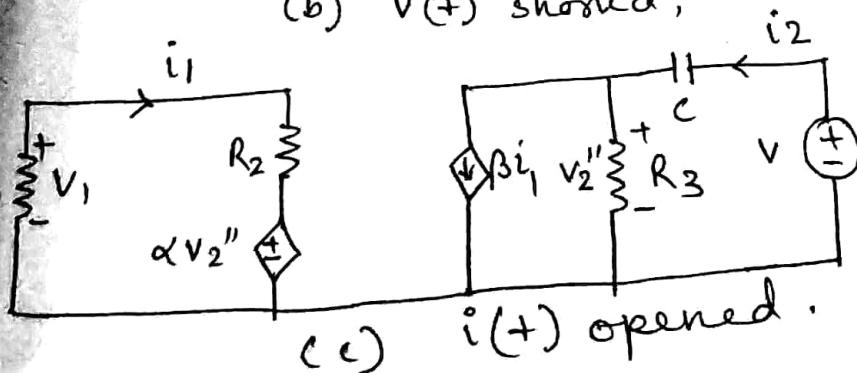

$i(+)$ opened.

Set $v(+)=0$. Let $V_1(s) = hV_1(+)$
 KCL and KVL equations are as follows:

$$I(s) = \frac{V_1(s)}{R_1} + I_1(s)$$

$$V_1(s) = \alpha V_2'(s) + R_2 I_1(s)$$

$$V_2'(s) = -\beta I_1(s) \cdot \frac{1}{1/R_3 + sc}$$

values, $I_1(s)$, $V_1(s)$ and substituting parameters

$$V_2'(+) = h^{-1} V_2''(s) = h^{-1} - \frac{1}{2} \left(-\frac{1}{s+0.5} \right) \left(\frac{1}{s^2+1} \right)$$

$$= -\frac{2}{5} e^{-0.5t} - \frac{1}{\sqrt{s}} \sin(t - 63^\circ)$$

Set $i(+)=0$.

We get KCL and KVL equations as

$$V(s) = \frac{I_2(s)}{sc} + V_2''(s)$$

$$\frac{V_2''(s)}{R_3} = I_2(s) - \beta I_1(s)$$

$$I_1(s) = -\frac{\alpha V_2''(s)}{R_1 + R_2}$$

Eliminating $I_1(s)$ and $I_2(s)$ and substituting values,

$$V_2''(+) = h^{-1} V_2''(s) = h^{-1} \left(\frac{s}{s+2} \right) \frac{1}{s^2+1}$$

$$= \left(\frac{1}{4} e^{-2t} + \frac{t}{2} - \frac{1}{4} \right)$$

Then, the total solution,

$$v_2(+) = V_2'(+) + V_2''(+)$$

$$= \left[-\frac{2}{5} e^{-0.5t} + \frac{1}{4} e^{-2t} - \frac{1}{4} - \frac{1}{\sqrt{s}} \sin(t - 63^\circ) \right]$$

Norton theorem
 equivalent
 as done in
 resistance
 however, in
 current
 resistance
 equivalent
 resistance

Statement

A linear dependent network consisting of the circuit the load - ce of load

Explanation

Norton

obvi

Next

Source

$(s) = h(s)$ follows:

NORTON'S THEOREM

Statement (with diagram).

Norton's Theorem is converse of Thvenin's Theorem. It consists of equivalent current source instead of equivalent voltage source as done in Thvenin's Theorem. The determination of internal resistance of the source network is identical in both theorems. However, in final stage, i.e., in the Norton equivalent circuit, the current generator is placed in parallel to the internal resistance unlike to that in Thvenin's Theorem where the equivalent voltage source was placed in series with the internal resistance.


Statement:

A linear active network consisting of independent and/or dependent voltage and current sources and linear bilateral network elements can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance, the current source being the short circuited current across the load terminal and the resistance being the internal resistance of the source network looking through the open circuited load terminals.

Explanation:

In order to find the current through r_L , the load resistance, by Norton's Theorem, let us replace r_L by short circuit (fig(a)).

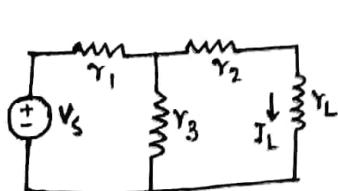
$$\text{Obviously, } i = \frac{V_s}{r_1 + \frac{r_2 r_3}{r_2 + r_3}} \quad \text{and } i_{s.e} = i \cdot \frac{r_3}{r_2 + r_3}$$



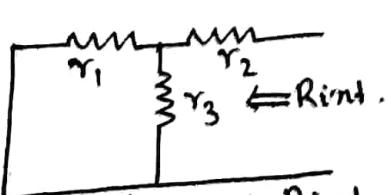(a) finding of $i_{s.e.}$.


Next, the short circuit is removed and the independent source is deactivated as done in Thvenin's Theorem. [fig.(b)].

$$\text{Here } R_{int} = r_2 + \frac{r_1 r_3}{r_1 + r_3}$$



(b). finding of R_{int} .

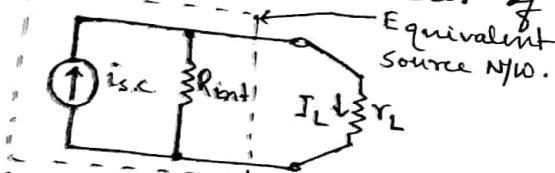As per Norton's theorem, the equivalent source circuit contain a current source in parallel to the internal ^{problems} resistance of the current source being the short circuited current at the shorted terminals of the load resistor [fig. (c)].



(c) Norton's Equivalent Circuit.

It may be noted here that determination of R_{int} for source system in Norton Theorem is identical to that of Thévenin's Theorem.

Steps for Solving a N/I/O using Norton's Theorem:

Step 1: Remove the load resistor and find the internal resistance of the source network by deactivating the constant current source. Let this resistance be R_{int} [same as R_{Th}].

Step 2: Next, short the load terminals and find the short current flowing through the shorted load terminals using conventional network analysis. Let this be i_{sc} .

Step 3: Norton's Equivalent circuit is drawn by keeping R_{int} in parallel to i_{sc} . as shown in fig. (c).

Step 4: Reconnect the load resistor (R_L) across the load and the current through it (I_L) is then given by

$$I_L = i_{sc} \cdot \frac{R_{int}}{R_{int} + R_L}$$

Obviously $I_L = i_{sc} \cdot \frac{R_{int}}{R_{int}}$


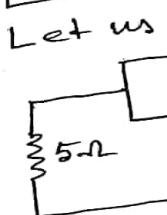


Fig. (a)

Here, R_{int} = 5Ω

To determine
looking
as shown

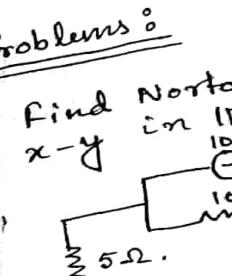


Here
Norton

Here

re circuit
internal
d current
[fig. (c)].
 $= I_{sc} \cdot R_{int}$

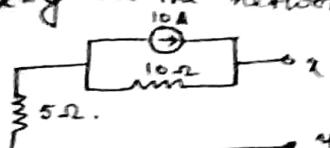Problems:

To find Norton's Equivalent circuit to the left of terminals x-y in the network shown.



Let us first short the terminals x-y


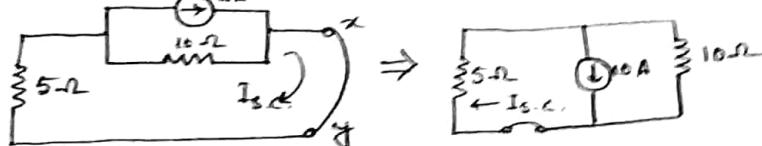
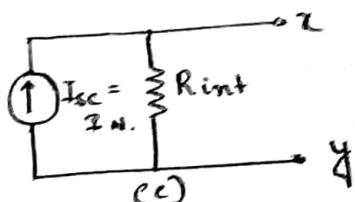


Fig. (a)

Here, I_{sc} is the current through the 5Ω resistor.
 $\therefore I_{sc} = 10 \times \frac{10}{10+5} = 6.67 \text{ A.}$ [by ct. divider rule].

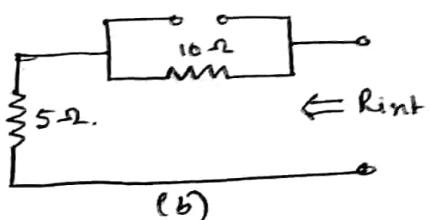To determine the equivalent resistance of the circuit, looking through x-y, the constant source is deactivated as shown in fig. (b).



(b)

$$\text{Hence } R_{int} = 10 + 5 = 15 \Omega.$$

Norton's Equivalent circuit has been shown in fig. (c).

$$\text{Hence } I_N = 6.67 \text{ A, } R_{int} = 15 \Omega.$$

Q. In the circuit if $R_1 = R_2 = 4\Omega$, find the short current i_{sc} across terminals $x-y$ using Norton's Theorem. What will happen if $R_1 = 2R_2$.



Application of KCL at node 1, yields

$$2 + 2i - 1 - i_{sc} = 0 \\ \text{i.e. } 2 + 2 = i_{sc} \quad \dots \dots \textcircled{1}$$

Application of KVL in the circuit

$$i_{sc}R_1 - iR_2 = 0$$

$$\text{Provided } R_1 = R_2, i_{sc} = i \quad \dots \dots \textcircled{2}$$

Using the value of $i (= i_{sc})$ in (1), we get

$$i_{sc} = 0 \text{ A.}$$

This shows that Norton Equivalent Circuit can be drawn for the given fig.

In case $R_1 = 2R_2$, we find from

$$i_{sc}R_1 - iR_2 = 0$$

$$2i_{sc}R_2 - iR_2 = 0$$

$$\text{or, } R_2(2i_{sc} - 1) = 0 \quad \dots \dots \textcircled{3}$$

However, R_2 is not equal to zero. Thus from (3)


$$2i_{sc} - i = 0$$

$$\text{or, } 2i_{sc} = i$$


Thus from (1) $i_{sc} = -2A$.

Norton Theorem is then applicable in the given p provided $R_1 \neq R_2$.

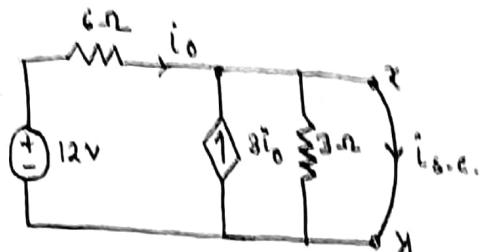Find the current through R_L in the circuit of fig using Norton's Theorem.



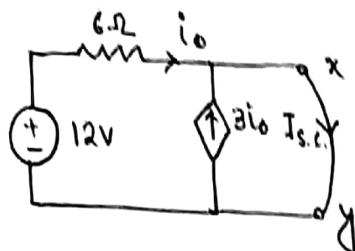Let us first remove R_L from x-y terminals and short x-y.




It is evident from fig.

$$I_{S.C.} = 3i_o + i_o = 4i_o$$

$$\text{But } i_o = \frac{12}{6} = 2 \text{ A.}$$

$$\therefore I_{S.C.} = 4 \times 2 = 8 \text{ A}$$

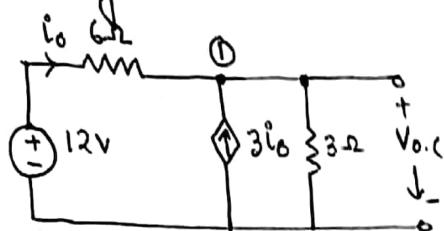Let us now remove the short circuit and it is open circuited at x-y.



Nodal Analysis at node 1 gives,

$$i_o + 3i_o - \frac{V_{O.C.}}{3} = 0$$


$$\text{or, } 4i_o - \frac{V_{O.C.}}{3} = 0$$

$$\text{or, } 4\left(\frac{12-V_{O.C.}}{6}\right) - \frac{V_{O.C.}}{3} = 0$$

$$\text{or, } 8 - \frac{2V_{O.C.}}{3} - \frac{V_{O.C.}}{3} = 0$$

$$\text{or, } V_{O.C.} = 8 \text{ V.}$$
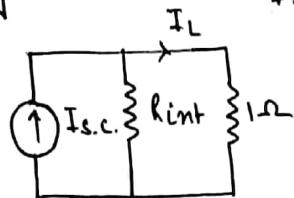
$$\text{This gives } R_{int} = \frac{V_{O.C.}}{I_{S.C.}} = \frac{8}{8} = 1 \Omega.$$




Norton's Equivalent Circuit

I_L (current through 1 Ω resistor)


$$= I_{S.C.} \cdot \frac{R_{int}}{R_{int} + R_L} = 8 \cdot \frac{1}{1+1} = 4 \text{ A.}$$

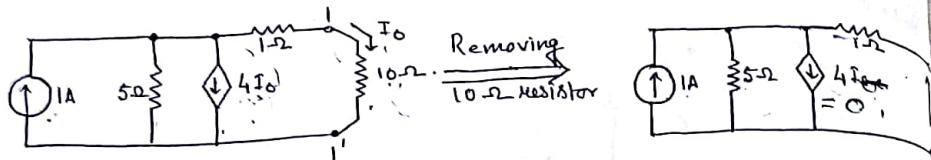4. Find the power loss in the 10Ω resistor in the circuit by Norton's Theorem.



$$V_{o.c} = (V_{1-1}) = 1 \times 5 = 5 \text{ V.}$$

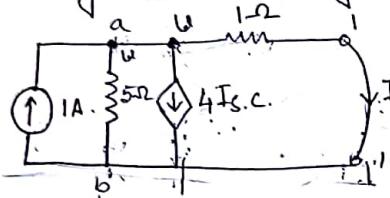Next short circuiting x-y terminals and assuming voltage at 'a' being U , nodal analysis yields.



$$I = \frac{U}{5} + 4I_{sc} + I_{sc}$$

$$\text{or, } 5I_{sc} + \frac{U}{5} = 1 \dots \dots \dots \textcircled{1}$$

$$\text{Also } I_{sc} = \frac{U}{1} = 5 \text{ A.}$$

$$\text{From (1)} \quad 5I_{sc} + \frac{I_{sc}}{5} = 1$$


$$\text{or, } I_{sc} = 0.1923 \text{ A.}$$

$$\text{This gives } R_{int} = \frac{V_{o.c}}{I_{sc}} = \frac{5}{0.1923} = 26 \Omega.$$

Thus Norton Equivalent Circuit is given by

$$I_{sc} = 0.1923 \text{ A.}$$


$$R_{int} = 26 \Omega.$$

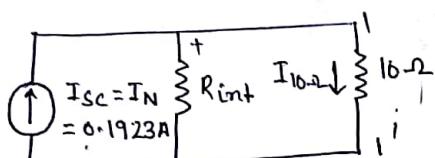


$$I_{10\Omega} = I_{sc} \cdot \frac{R_{int}}{R_{int} + 10} = 0.14 \text{ A.}$$

$$\therefore \text{Power Loss in the } 10\Omega \text{ resistor} = (I_{10})^2 \times 10 \\ = 0.195 \text{ W.}$$

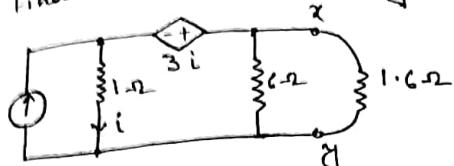Find the current through 1.6Ω resistor in the ckt.



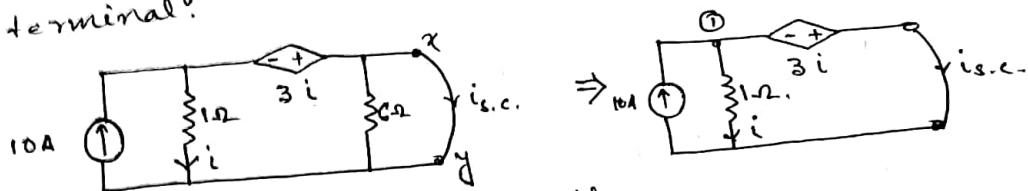Let us first remove the 1.6Ω resistor and short $x-y$ terminal.



Let node voltage at (1) be v volts.
 $i = \frac{v}{1} = v \text{ A}, \dots (1)$


KCL at node 1.

$$i_0 = i + i_{sc} \dots (2)$$

Also KVL at right loop yields, $v - 3i = 0$ or, $v = 3i \dots (3)$

Comparison of (1) and (3) yields that these eqns are only valid if $v = i = 0$.

This gives $i_{sc} = 10 \text{ A}$.

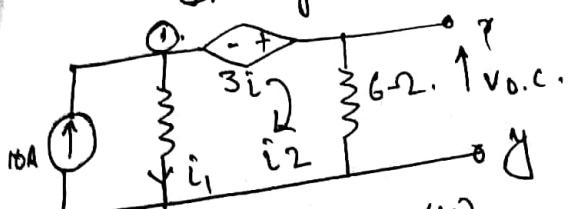

$$\text{At node } 1, 10 = i_1 + i_2 \dots (4)$$

$$i_2 = \frac{v + 3i_1}{0.6}$$

$$i_2 = \frac{i_1 \times 1 + 3i_1}{0.6} = \frac{2}{3} i_1$$

Thus from eqn. (4), $i_1 + \frac{2}{3} i_1 = 10, i_1 = 6 \text{ A}$.

$$i_1 + \frac{2}{3} i_1 = 10, i_1 = 6 \text{ A}$$


$$\text{Also, } V_{o.c} = i_2 \times 0.6 = (10 - i_1) \times 0.6 = 24 \text{ V}$$

$$\text{Hence } R_{int} = \frac{V_{o.c}}{I_{sc}} = \frac{24}{10} = 2.4 \Omega$$

Current through 1.6Ω resistor is.

$$I(1.6\Omega) = I_{sc} \cdot \frac{R_{int}}{R_{int} + 1.6} = 10 \cdot \frac{2.4}{2.4 + 1.6} = 6 \text{ A}$$

Find Norton's Equivalent Circuit for the network shown.
Assume $I = 5 \angle 0^\circ A$.

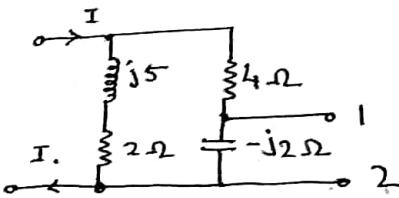

Terminals 1-2 are shorted. No current would flow through $(-j2\Omega)$ capacitive reactance due to shorting of terminal 1-2.


Obviously,

$$I_{s.c} = \frac{(2+j5)}{(2+j5+4)} \times I = \frac{5 \angle 0^\circ (2+j5)}{6+j5}$$

$$= \frac{10+j25}{6+j5} = \frac{26.926 / 68.198^\circ}{7.81 L 39.81^\circ}$$

$$= 3.45 L 28.39^\circ A$$

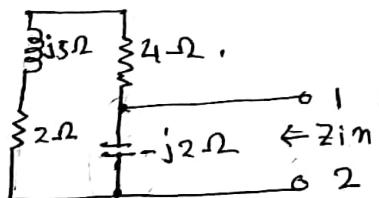
Internal impedance can be obtained by deactivating the current source.




$$Z_{in} = \frac{-j2(4+2+j5)}{-j2+4+j5+2} = \frac{-j8-j4+10}{6+j3}$$

$$= \frac{10-j12}{6+j3} = \frac{15.62 L -50.19^\circ}{6.71 L 26.56^\circ}$$

$$= 2.33 L -76.75^\circ \Omega$$

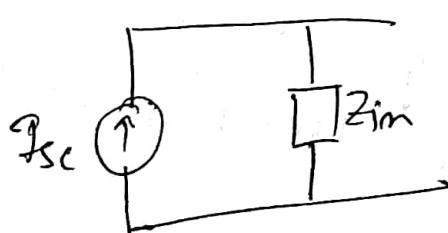

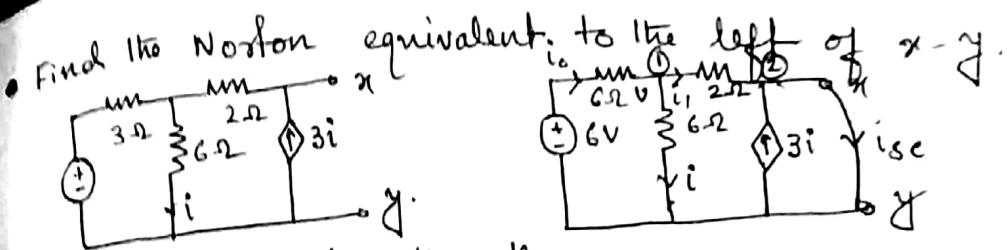


$$\text{At node 1}, \frac{v-6}{3} + \frac{v}{6} + \frac{v}{2} = 0,$$

$$\text{or, } v = 2V, \text{ this gives } i = v/6 = 1/3 A.$$

$$i_0 = -\frac{v-6}{3} = -\frac{2-6}{3} = 4/3 A., i_1 = i_0 - i = \frac{4}{3} - 1/3 = 1A.$$

At node 2: $i_1 + 3i = I_{SC}$, $\therefore I_{SC} = 1 + 3 \times 1/3 = 2A$.

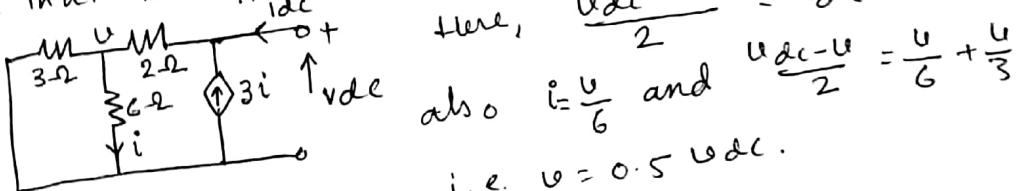To find R_{int} $x-y$ is open circuited and the cont. source is deactivated. A de. voltage V_{dc} is applied such that the i/p ext. is $2 \cdot i_{dc}$.



$$\text{Here, } \frac{V_{dc}-v}{2} = i_{dc} + 3i$$

$$\text{also } i = \frac{v}{6} \text{ and } \frac{V_{dc}-v}{2} = \frac{v}{6} + \frac{v}{3}$$

$$\text{i.e. } v = 0.5 V_{dc}.$$


$$\text{Thus, } i = \frac{v}{6} = \frac{0.5 V_{dc}}{6} = \frac{0.5 V_{dc}}{6}$$

$$\text{Then } \frac{V_{dc}-v}{2} = i_{dc} + 3 \cdot \frac{0.5 V_{dc}}{6} = i_{dc} + 0.5 V_{dc}$$

$$\text{or, } i_{dc} = 0, \therefore R_{int} = \frac{V_{dc}}{i_{dc}} = \infty \Omega$$

$$\text{Thus } R_{int} = \infty \Omega, I_{SC} = I_N = 2A.$$

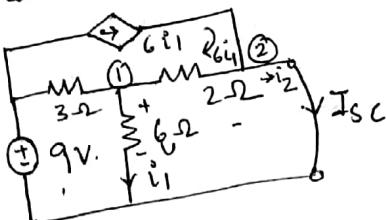Find Norton's Equivalent to the left of $x-y$.



$$\text{Here, } i_1 = v/6.$$

$$\text{At } ① \quad i_2 + 6i_1 = I_{SC}. \quad [\because i_2 = 1/2]$$

$$\text{or, } v/2 + 6 \cdot v/6 = I_{SC}.$$

$$\text{or, } 3/2 v = I_{SC}, \text{ i.e. } I_{SC} = 1.5 v.$$

$$\text{Again at Node } ① \quad \frac{v-9}{3} + \frac{v}{6} + \frac{v}{2} = 0,$$

$$v = 3V, \text{ thus } I_{SC} = 1.5 \times 3 = 4.5A = I_N.$$

$$\text{To find } \frac{V_{oc}}{I_{sc}}, \text{ open } x-y: \quad i_1 = 6i_1 \Rightarrow \cancel{i_1} = \frac{v_1}{3} - 3 - 5i_1 = 0.$$

$$\text{At } ① \quad \frac{v_1 - 9}{3} + i_1 = 6i_1 \Rightarrow$$

$$\text{But } i_1 = v_1/6 A.$$

$$\therefore \frac{v_1 - 9}{3} - 3 - \frac{5}{6} v_1 = 0$$

$$\text{Thus we get, } \frac{v_1}{3} - 3 - \frac{5}{6} v_1 = 0$$


$$\text{or, } v_1 = -6V.$$

$$\text{However, } V_{oc} = v_1 + (2 \cdot 2 \times 6i_1) = v_1 + 12i_1$$


$$= v_1 + 12 \cdot \frac{v_1}{6} = 3v_1 = -18V$$

$$\text{Thus } R_{int} = \frac{V_{oc}}{I_{sc}} = 4 \Omega.$$

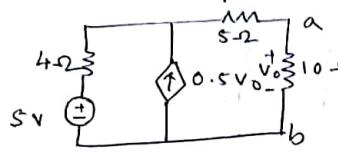- what is the power loss in the 10Ω resistor of the circuit?



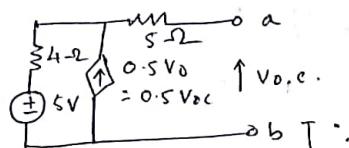Let us first remove the 10Ω resistor from a-b terminals. In the left most loop, the circulating current will obviously be $(0.5V_0)A$.



Applying KVL in the leftmost loop,

$$5 - (-0.5V_0) \times 4 = V_{o.c.}$$

\therefore The ct. $(0.5V_0) A$ is anticlockwise causing voltage drop additive to the 5V source, also, current thru 5Ω resistor being nil, $V_{o.c}$ is the voltage drop across x-y terminals.

$$\therefore V_{o.c} = 5 + 2V_0 \quad \text{But with ref. to fig. (2),}$$

$$V_{o.c} = V_{o.c} \quad \text{from (1) } V_{o.c} = -5V \quad [b \text{ is +ve}].$$

From fig. (b), a-b is shorted. it is evident that $0.5V_0 = 0$, as there is no drop across short path.

$$\text{I}_{sc} = \frac{5}{(4+5)\Omega} = 5/9 A.$$

$$\text{Thus } R_{int} = (R_{th}) = \frac{V_{o.c}}{I_{sc}} = \frac{5}{5/9} = 9\Omega.$$

[$-ve$ sign of $V_{o.c}$ is neglected].

Thus, following Thévenin's equivalent ckt.

I_{th} = ct. thru. 10Ω resistor,

$$= \frac{V_{o.c}}{R_{int} + 10} = \frac{5}{9+10} = 5/19 A. \quad [\because V_{o.c} \text{ is } -ve, I_{th} \text{ will flow from } b \text{ to } a].$$

Power in 10Ω resistor is $(5/19)^2 \times 10$ i.e. 692.5 mW .

Find the
the load



Remov
be Appy



APP
It at
to

i.e.


of $\frac{1}{L}$ circuit
The 10Ω
resistor in $\frac{1}{L}$
circuiting in $\frac{1}{L}$
 $0.5V_1$ across
loop.

choose
 V_o ,
voltage

& that


allow

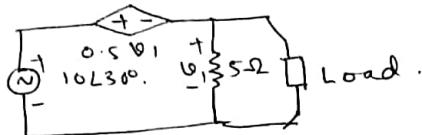Find the Thevenin's eq. n/w. for the net shown across the load.



Removing the load, assuming the open ckt. voltage to be V_{oc} , it is seen that $V_{oc} = V_1$. Applying KVL in the left loop of fig. (a).

$$-10L30^\circ + 0.5V_1 + V_1 = 0$$

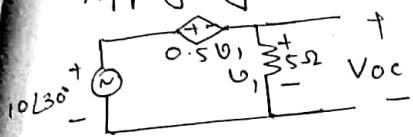

$$\text{or, } 1.5V_1 = 10L30^\circ$$

$$\therefore V_1 = 6.67 L30^\circ \text{ V } (= V_{oc})$$

Applying short circuit across the opn., it is clear that $V_1 = 0$. This makes the dependent source also to be zero. $I_{sc} = \frac{10L30^\circ}{0}$ [∴ there is no other impedance in the loop]

$$\text{i.e. } I_{sc} = \infty, Z_{int} = \frac{V_{oc}}{I_{sc}} = \frac{V_{oc}}{\infty} = 0\Omega$$

Maximum Power Transfer Theorem

This theorem is used to find the value of load resistance for which there would be maximum amount of power transfer from source to load.

Statement:

A resistance load, being connected to a d.c. network, receives maximum power when the load resistance is equal to the internal resistance (Thevenin's Equivalent resistance) of the source network as seen from the load terminals.

Explanation:

A variable resistance R_L is connected to a d.c. source network as shown in fig. (a) while fig. (b) represents the Thevenin voltage V_0 and Thevenin resistance R_{Th} of the source network. The aim is to determine the value of R_L such that it receives maximum power from the d.c. source.

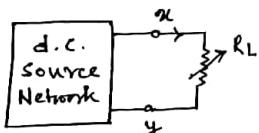


Fig. (a)

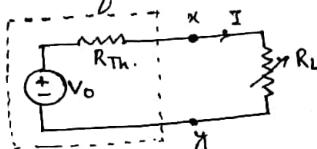


Fig. (b).

With reference to fig. (b), $I = \frac{V_0}{R_{Th} + R_L}$

while the power delivered to the resistive load is,

$P_L = I^2 R_L = \left(\frac{V_0}{R_{Th} + R_L} \right)^2 \times R_L$.
 P_L can be maximised by varying R_L and hence, maximum power can be delivered when $(\frac{\partial P_L}{\partial R_L}) = 0$.

However,

$$\frac{dP_L}{dR_L} = \frac{1}{[(R_{Th} + R_L)^2]^2} \left[(R_{Th} + R_L)^2 \frac{d}{dR_L} (V_0^2 R_L) - V_0^2 R_L \frac{d}{dR_L} (R_{Th} + R_L)^2 \right]$$

$$= \frac{1}{(R_{Th} + R_L)^4} \left[(R_{Th} + R_L)^2 V_0^2 - V_0^2 R_L \times 2(R_{Th} + R_L) \right]$$

$$= \frac{V_0^2 (R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3}$$

$$= \frac{V_0^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3}$$

$$\text{But } \frac{dP_L}{dR_L} = 0$$

$$\therefore \text{Finally, } \frac{V_o^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3} = 0$$

which gives $(R_{Th} - R_L) = 0$ or $R_{Th} = R_L$.

Hence, it has been proved that power transfer from a d.c. network to a resistive network is maximum when the internal resistance of the d.c. source network is equal to the load resistance.

Again, with $R_L = R_{Th}$, the system being perfectly matched and source, the power transfer becomes maximum and amount of power (P_{max}) can be obtained as

$$P_{max} = \frac{V_o^2 R_{Th}}{(R_{Th} + R_L)^2}$$

$$= \frac{V_o^2 / 4 R_{Th}}{=}$$

It may be noted that this is the power consumed by the load. Obviously, the power transfer by the source would be also $V_o^2 / 4 R_{Th}$, the load power and source power being the same.

$$\text{The total power supplied is thus } P = 2 \frac{V_o^2}{4 R_{Th}} = \frac{V_o^2}{2 R_{Th}}$$

During maximum power transfer the efficiency η becomes

$$\eta = \frac{P_{max}}{P} \times 100 = 50\%$$

The concept of maximum power transfer by small source resistance is widely applied in communication circuits where the magnitude of power transfer is sufficiently small. To achieve maximum power transfer, then the source and load resistances are matched and with flow of maximum power from source to load, low efficiency of 50% is tolerated. On the other hand, in electric power transmission systems, the load resistance being sufficiently greater than the source resistance, it is difficult to achieve the maximum power transfer ordinarily. Moreover in power transmission systems emphasis is given to keep voltage drops and line losses to a minimum value and hence operation of the system, operating with bulk power transmission becomes uneconomical if it be operated with only 50% just for the sake of max. power transfer. Hence in power transmission system this criterion of max. power transfer is not realized.

Steps for Solution:

Step 1: Remove the load resistance and find Thevenin's Resistance (R_{TH}) of the source network looking through the open circuited load terminals.

Step 2: As per maximum power transfer theorem, this R_{TH} is the load resistance of the network i.e. $R_L = R_{TH}$ that follows maximum power transfer.



Step 3: Find the Thevenin's Voltage (V_o) across the open circuited load terminals.

Step 4: Maximum power transfer is given by:

$$\frac{V_o^2}{4R_{TH}}$$

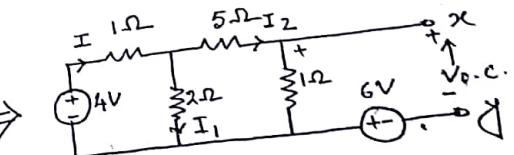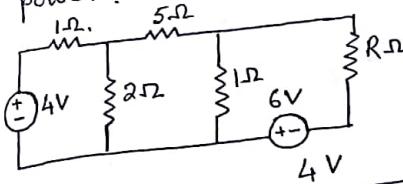Example:

Find the value of R in the circuit of fig. such that maximum power transfer takes place. What is the amount of this power?



$$\text{Here } I = \frac{[\{ (5+1) / 2 \} + 1] \cdot 1}{5/2} = \frac{4}{5/2} = \frac{8}{5} \text{ A.}$$

$$\therefore I_2 = I \frac{2}{2+5+1} = \frac{8}{5} \times \frac{1}{4} = \frac{2}{5} \text{ A.}$$

The drop across a-b branch is then,
 $V_{a-b} = \frac{2}{5} \times 1 = \frac{2}{5} \text{ V.}$


$$\text{Obviously, } V_{o.c} = V_{a-b} + 6V = \frac{2}{5} + 6 = \frac{32}{5} \text{ V.}$$

$$\text{or, } V_{o.c} = 6.4 \text{ V.}$$

$$R_{TH} = (1112 + 5) / 111 = \frac{17}{3} / 111 = \frac{17}{20} \Omega$$


$$= 0.85 \Omega.$$

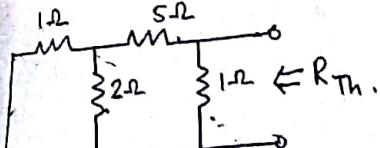As per max. power transfer $R = R_{TH} = 0.85 \Omega$.
 $\text{and } P_{max} = \frac{V_{o.c}^2}{4R} = \frac{(6.4)^2}{4 \times 0.85} = 12 \text{ Watt.}$




Maximum Power Transfer

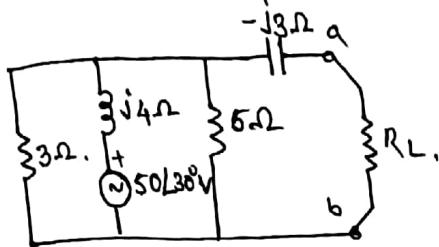What should be the value of R_L so the maximum power can be transferred from the source to R_L .



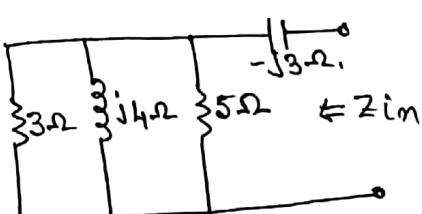Sol. Removing R_L , deactivating the source, the internal impedance can be found out as follows.



$$\begin{aligned} Z_{int} &= (-j3) + \frac{1}{1/5 + 1/3 + 1/j4} \\ &= (-j3) + \frac{1}{0.2 + 0.33 - j0.25} \\ &= \left[-j3 + \frac{1}{(0.533 - j0.25)} \right] \Omega. \\ &\quad : (1.54 - j2.28) \Omega. \end{aligned}$$

Current from $50 L 30^\circ V$ source is, $= 2.75 L - 56^\circ A.$

$$I = \frac{50 L 30^\circ}{j4 + \frac{5 \times 3}{5+3}} A = 11.32 L - 34.89^\circ A.$$


$$\therefore V_{o.c} = I \times \frac{9}{3+5} = 11.32 \times 3/8$$

$Z_{int} \cdot R_L = \text{Real Part of } Z_{int} = 1.54 \Omega.$

$$P_{max} = \frac{V_{o.c}^2}{4R_L}$$

$$= \frac{50 L 30^\circ}{4 \cdot 417 L 64.88} = 11.31 L - 34.88^\circ$$

$$I = \frac{50 L 30^\circ}{j4 + 1.54}$$

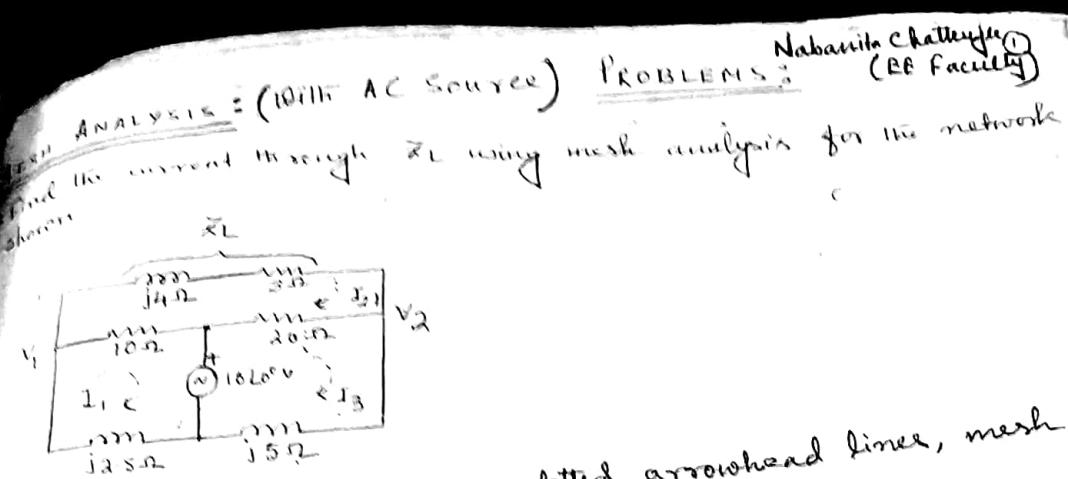

The mesh eq. being given by dotted arrowhead lines, mesh analysis gives.

$$(10 + j2.5)I_1 - 10I_2 = -10L0^\circ \dots \dots \dots (1)$$

$$(20 + j5)I_3 - 20I_2 = 10L0^\circ \dots \dots \dots (2)$$

$$(33 + j4)I_2 + I_2(33 + j4) = 0 \dots \dots \dots (3)$$

Rearranging in matrix form,


$$\begin{bmatrix} (10 + j2.5) & -10 & 0 \\ 0 & -20 & (20 + j5) \\ -10 & (33 + j4) & -20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -10L0^\circ \\ 10L0^\circ \\ 0 \end{bmatrix}$$

$$\therefore I_2 = \frac{\begin{vmatrix} 10 + j2.5 & -10L0^\circ & 0 \\ 0 & 10L0^\circ & 20 + j5 \\ -10 & 0 & -20 \end{vmatrix}}{\begin{vmatrix} 10 + j2.5 & -10 & 0 \\ 0 & -20 & (20 + j5) \\ -10 & (33 + j4) & -20 \end{vmatrix}} = \frac{(10 + j2.5)10L0^\circ \times (-20) - (-10L0^\circ)}{(10 + j2.5)(10L0^\circ)^2 - 10(20 + j5)^2}$$

where $A_Z = \text{determinant of the matrix in the denominator.}$

$$= \frac{-2000 - j500 + 2000 + j500}{A_Z} = \frac{0}{A_Z} = 0.$$

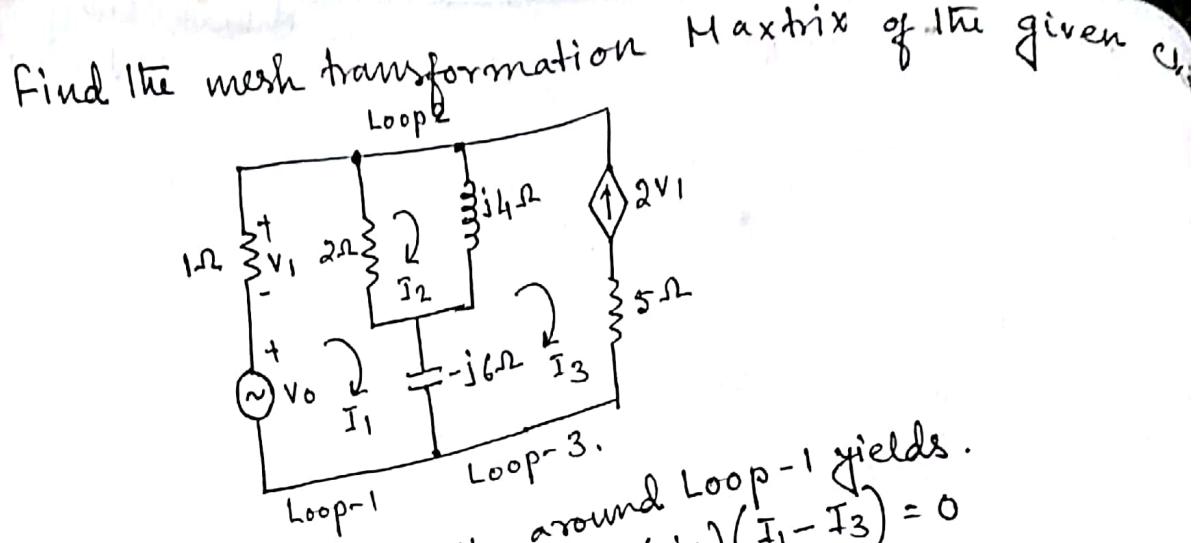Thus it is seen that no current would flow through Z_L , since I_2 is found to be zero and at the starting of the solution, I_2 had been the current flowing through Z_L .



Sol. Application of KVL around Loop -1 yields.

$$+V_0 - 1 \cdot I_1 - 2(I_1 - I_2) - (-j6)(I_1 - I_3) = 0$$

$$+V_0 - I_1(3 - j6) + 2I_2 - j6 \cdot I_3 = -V_0.$$

$$\text{or, } -I_1(3 - j6) + 2I_2 - 2I_2 + j6I_3.$$

$$\text{or, } V_0 = I_1(3 - j6) - 2I_2 + j6I_3.$$

Application of KVL at loop -2 yields.

$$-2(I_2 - I_1) - j4(I_2 - I_3) = 0$$

$$-2(I_2 - I_1) - j4I_2 + (j4)I_3 = 0.$$

$$\text{or, } -2I_1 + I_2(2 + j4) - (j4)I_3 = 0.$$

Presence of current source in the third loop makes the KVL redundant and using KCL.

$$I_3 = -2V_1 = -2I_1$$


$$\text{or, } I_3 + 2I_1 = 0.$$

Thus,

$$\begin{bmatrix} (3 - j6) & -2 & +j6 \\ -2 & (2 + j4) & (-j4) \\ 2 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_0 \\ 0 \\ 0 \end{bmatrix}$$



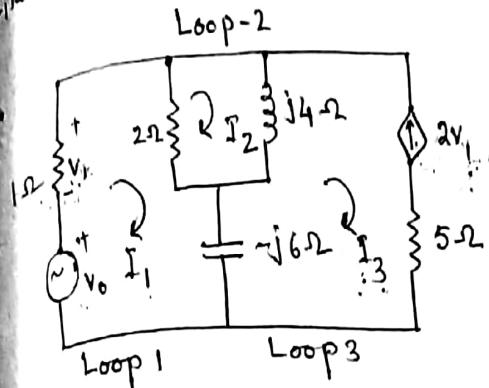Find the mesh transformation matrix of the given circuit.



Application of KVL around Loop-1 yields

$$V_0 - I_1 \cdot Z_1 + 2(I_1 - I_2) - (-j6)(I_1 - I_3) = 0 \quad (1)$$

$$v_o = -I_1(3 - j6) + 2I_2 - j6 \cdot I_3 = v_o \quad \text{--- (1)}$$

KVL at loop-2 yields.

$$-2(I_2 - I_1) - j4(I_2 - I_3) = 0 \quad \dots \quad (2)$$

or, $2I_1 - I_2(2+j4) + (j4)I_3 = 0$... in the third loop makes the use of

Presence of current source in the third loop makes the use of KVL redundant and using KCL,
 $I_3 = -2V_1 = -2I_1$ (3).

$$I_2 = -2V_1 = -2\overline{I}_1 \quad (3)$$

$$m_1 I_3 + 2I_1 = 0$$

In matrix form.

$$\begin{matrix} \text{In matrix form:} \\ \left[\begin{array}{ccc|c} 3-j6 & -2 & +j6 & f_1 \\ 2 & -(2+j4) & -j4 & f_2 \\ 2 & 0 & 1 & f_3 \end{array} \right] = \left[\begin{array}{c} v_b \\ 0 \\ 0 \end{array} \right] \end{matrix} \quad \begin{aligned} &+ 2(2+j8) + j6(4+j6) \\ &= -6 - j12 + 12j - 24 + 4 + 16j \\ &\quad + 24j - 48 \\ &= -74 + 40j \end{aligned}$$

\downarrow
Mesh Transformation
Matrix.


$$\Delta_1 = \begin{bmatrix} v_c & -2 & +j6 \\ 0 & -(2+j4) & -j4 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= V_0 \left[-(2+j4) - 0 \right] \Rightarrow (5+j0)(-2-j4) = -10 - 20j + 0 \\ = -(10+20j).$$

$$I_1 = \frac{A_1}{A} , = \frac{-10 - 20j}{-74 + 40j} = \frac{22 \cdot 36 \angle -116.56}{44 \cdot 11 \angle 151.60} = 0.265 \angle$$

Say $V_0 = 5 L^{\circ}$.

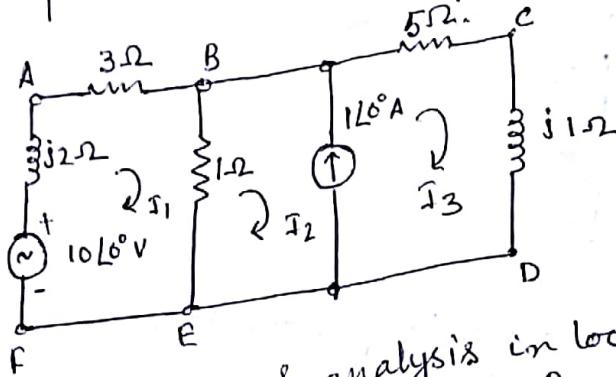Prob. Develop mesh equations for the network shown, the power absorbed by the 3Ω resistor.



Application of mesh analysis in loop AB EF yields:

$$I_1(4+j2) - I_2 \times 1 = 10∠0^\circ \dots \dots \dots (1)$$

$$\text{For loop BCDE, } (5+j1)I_3 + I_2 - I_1 = 0 \dots \dots \dots (2)$$

$$\text{or, } -I_1 + I_2 + (5+j1)I_3 = 0 \dots \dots \dots (3).$$

But it is evident from fig. $I_3 - I_2 = 1∠0^\circ$. \therefore from (1),

Next, subtracting equation (3) from (1),

$$(4+j2)I_1 - I_3 = 10∠0^\circ - 1∠0^\circ$$

$$= 9. \quad \dots \dots \dots (4)$$

or, $I_3 = [(4+j2)I_1 - 9]$. \therefore we get,

$$\text{Also adding equation (1) to (2), we get, } (4+j2)I_1 - I_1 + (5+j1)I_3 = 10∠0^\circ.$$

$$(4+j2)I_1 - I_1 + (5+j1)[(4+j2)I_1 - 9] = 10.$$

$$\text{or, } (3+j2)I_1 + (5+j1)[(4+j2)I_1 - 9(5+j1)] = 10$$

$$\text{or, } 3I_1 + j2I_1 + (5+j1)(4+j2)I_1 - 9(5+j1) = 10$$

$$\text{or, } 3I_1 + j2I_1 + 20I_1 + j16I_1 + j4I_1 - 2I_1 - 45 - j9 = 10$$

$$\text{or, } 3I_1 + j2I_1 + 20I_1 + j16I_1 = 10 + 45 + j9$$

$$\text{or, } 21I_1 + j16I_1 = 55 + j9.$$

$$= 55 + j9.$$


$$I_1 = \frac{55 + j9}{21 + j16} = \frac{55 + j9}{26.4} L 9.29^\circ$$

$$= 2.11 L -28.01^\circ A.$$

Power absorbed by 3Ω resistor is,

$$(2.11)^2 \times 3 = 13.36 \text{ Watt.}$$

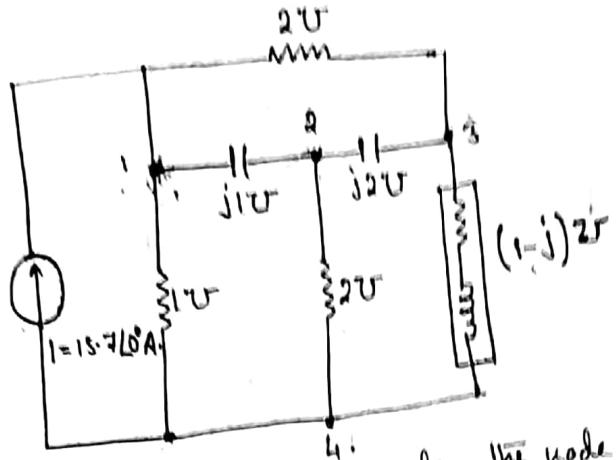Calculate the Power Delivered by the source in the circuit.



Taking Node 4 as the datum node, the node equations are,

$$\text{Node 1: } V_1(1+2+j1) - jV_2 - 2V_3 = 15.7 \angle 0^\circ.$$

$$\text{Node 2: } -jV_1 + V_2(2+j1+j2) - 2jV_3 = 0$$

$$\text{Node 3: } -2V_1 - 2jV_2 + V_3(1-j1+j2+2) = 0.$$

Node 3:

In Matrix Form:

$$\begin{bmatrix} 3+j1 & -j & -2 \\ -j & 2+j3 & -2j \\ -2 & -2j & 3+j1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 15.7 \\ 0 \\ 0 \end{bmatrix}.$$

$$V_1 = \frac{\begin{vmatrix} 15.7 & -j & -2 \\ 0 & 2+j3 & -2j \\ 0 & -2j & 3+j \end{vmatrix}}{\begin{vmatrix} 3+j & -j & -2 \\ -j & 2+j3 & -2j \\ -2 & -2j & 3+j \end{vmatrix}} = \frac{15.7(7+11j)}{13+j29}.$$

Power Delivered by the source = $V_1 I \cos \theta = \text{Real}[V_1 I]$,
which on simplification equals 100 watts.


$V_1 I$ = Apparent Power

$$V_1 I \angle 0^\circ = r \cos \theta + j r \sin \theta.$$

$$r \angle 0^\circ = a + jb.$$

$$r = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1} b/a.$$

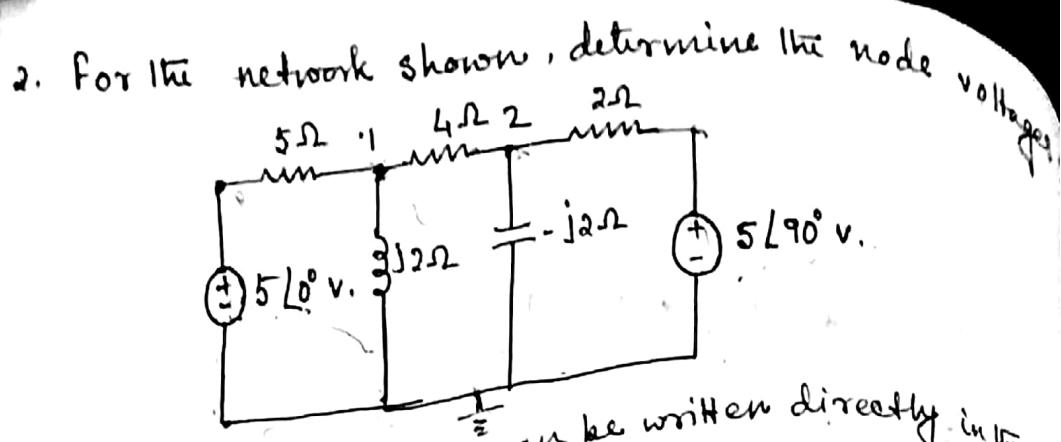


The nodal equations can be written directly in the after source transformation.

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{j2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{-j2} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{5}{5} \angle 0^\circ \\ \frac{5}{2} \angle 90^\circ \end{bmatrix} = \begin{bmatrix} 1 \\ j2.5 \end{bmatrix}$$

$$V_1 = \frac{1}{\Delta} \begin{vmatrix} 1 & -0.25 \\ j2.5 & 0.25 + j0.5 \end{vmatrix} = 3.44 \angle 26.47^\circ,$$

$$V_2 = \frac{1}{\Delta} \begin{vmatrix} 0.45 - j0.5 & 1 \\ -0.25 & j2.5 \end{vmatrix} = 0.545 \angle -15.8^\circ,$$
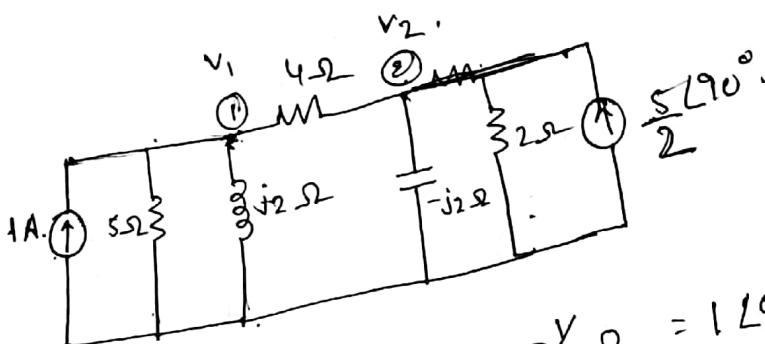
$$\text{where } \Delta = \begin{vmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{vmatrix}$$



$$\text{at node 1: } \frac{V_1}{5} + \frac{V_1}{j2} + \frac{(V_1 - V_2)}{4} = 1 \angle 0^\circ.$$


$$V_1 \left[\frac{1}{5} + \frac{1}{j2} + \frac{1}{4} \right] - \frac{V_2}{4} = 1 \angle 0^\circ.$$

$$\text{at node 2: } \frac{V_2}{-j2} + \frac{V_2}{2} + \frac{(V_2 - V_1)}{\frac{1}{4}} = \frac{5}{2} \angle 90^\circ$$

$$-\frac{1}{4}V_1 + V_2 \left[\frac{1}{2} + \frac{1}{4} + \frac{1}{-j2} \right] = 0 + j2.5.$$

Ques (Network Analysis)

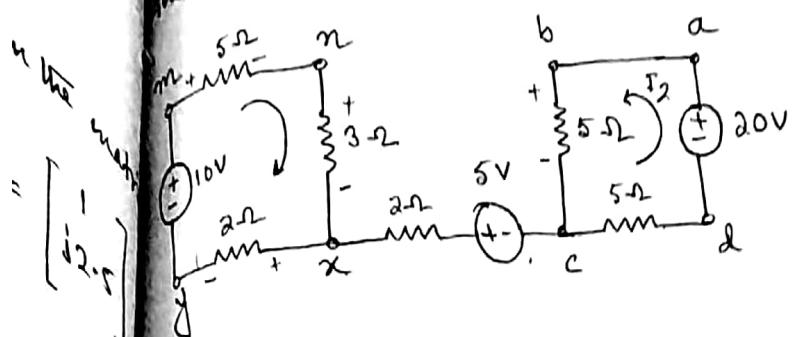and the drop between the terminals y and d in the network.



The current in loop $m-n-x-y$ is given by

$$I_1 = \frac{10}{5+2+3} = 1 \text{ A.}$$

Drop in $m-n$ branch $V_{m-n} = 5 \times 1 = 5 \text{ V.}$

Drop in $n-x$ branch $V_{n-x} = 3 \times 1 = 3 \text{ V.}$

Drop in $x-y$ branch $V_{x-y} = 2 \times 1 = 2 \text{ V.}$

Drop in $a-b-c-d$, $I_2 = \frac{20}{5+5} = 2 \text{ A.}$

Current in loop $a-b-c-d$, $I_2 = \frac{20}{5+5} = 2 \text{ A.}$

Drop in $b-c$, $V_{b-c} = 5 \times 2 = 10 \text{ V.}$


Drop in $c-d$, $V_{c-d} = 5 \times 2 = 10 \text{ V.}$

Drop in $x-y$ branch $V_{x-y} = 2 \times 1 = 2 \text{ V.}$

Impacting the respective polarities,

$$V_{y-d} = V_{y-x} + V_{x-c} + V_{c-d} = -2 + 5 + 10 = 13 \text{ V.}$$

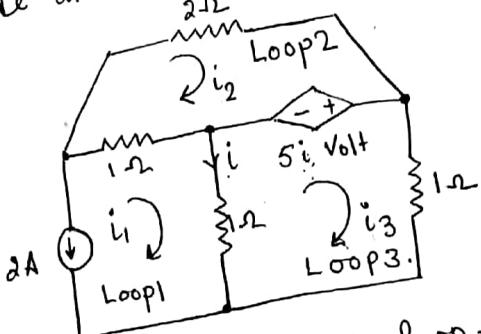Using Mesh Analysis, find the magnitude of the current dependent source and the current through the 2Ω resistor.



Sol. It is evident that in loop -1,

$$i_1 = -2 \text{ A.}$$

$$\text{In loop -3, } i_3 \times 1 + (i_3 - i_1) \cdot 1 - 5i = 0$$

$$\text{However, } i = i_1 - i_3$$

$$\text{and } i_1 = -2 \text{ A.}$$

Substituting these values

$$i_3 + (i_3 + 2) - 5(-2 - i_3) = 0$$
$$\text{or, } i_3 + i_3 + 2 + 10 + 5i_3 = 0$$
$$\text{or, } i_3 = -\frac{12}{7} = -1.71 \text{ A.}$$

In Loop -2,

$$i_2 \times 2 + 5i_1 + (i_2 - i_1) = 0$$
$$\text{or, } 2i_2 + 5(i_1 - i_3) + i_2 - i_1 = 0$$
$$\text{or, } 3i_2 + 4i_1 - 5(-1.71) = 0$$
$$\text{or, } 4i_1 + 3i_2 = -8.55$$
$$\text{or, } 4(-2) + 3i_2 = -8.55$$
$$\therefore i_2 = -0.183 \text{ A.}$$

$$\text{Also } i = i_1 - i_3 = -2 - (-1.71) = -0.29 \text{ A.}$$

Value of dependent source $= 5i = -5 \times 0.29 = -1.45$,

Thus the magnitude of dependent source $= 1.45 \text{ V}$

The magnitude of the actual current i which was found out, is upwards in the circuit, the actual polarity of dependent source is opposite to that shown.

The current through 2Ω resistor is i_2 i.e. 0.183 A flowing anticlockwise in loop -2.


The equivalent directed current
 $\frac{5 \times 2}{5+2} = \frac{10}{7} \text{ A}$
By curv

i.e. 1


Find v
The de

AP

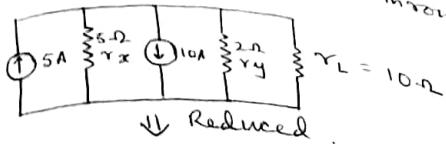and Mesh Analysis with DC source:
in the circuit find the current through r_L .



↓ Reduced.

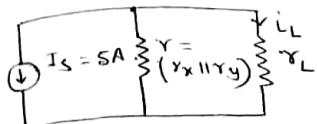


The equivalent current source I_S would be directed downwards, the net resistance of r_x and r_y would be $\frac{6 \times 2}{5+2} = \frac{10}{7} \Omega$.

By current division method

$$i_L = I_S \times \frac{r}{r+r_L} = 5 \times \frac{10/7}{10/7 + 10} = 5 \times \frac{10}{7} \times \frac{7}{80} = \frac{5}{8} A.$$

$$\text{i.e. } i_L = \frac{5}{8} A.$$

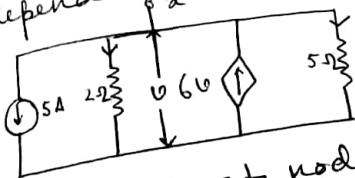Find v in the circuit. Also obtain numerical value of the dependent source.



Applying KCL at node 'x'.

$$-5 + 6v - \frac{v}{2} - \frac{v}{5} = 0$$


$$-5 + 6v - \frac{v}{2} - \frac{v}{5} = 0 \Rightarrow v = 0.943V.$$

$$\text{or, } \frac{53}{10} v = 5, \text{ or } v = \frac{50}{53} = 0.943V.$$

The numerical value of the dependent source is then

$$6 \times 0.943 = 5.66A$$

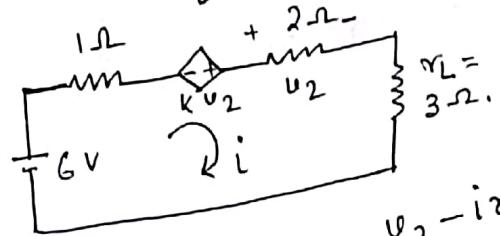3. In the circuit find the drop across r_L if $k = 2$.



$$\text{SOL} . \quad 6 - ix_1 + Ku_2 - u_2 - ir_L = 0$$

$$\text{or}, \quad 6 - i(1 + r_L) + u_2(k-1) = 0.$$

$$\text{or}, \quad 6 - 4i + u_2 = 0$$


$$\text{But, } u_2 = ix_2 = 2i.$$

$$\therefore 2i = 6$$

$$\text{or, } i = 3A.$$

$$\therefore \text{Drop across } r_L = 3 \times 3 = 9V. \text{ (with positive polarity)}$$

4. Find i and V_x in Fig.

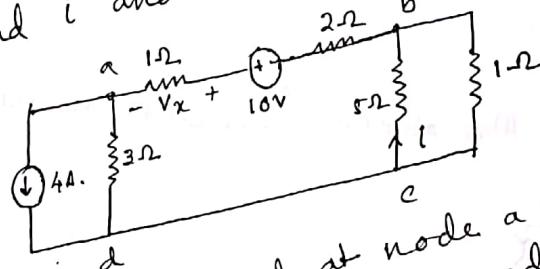

Sol. Let the potential at node a be V_a and b be V_b . Applying nodal analysis at node a ,

$$4 + \frac{V_a}{3} + \frac{V_a - 10 - V_b}{3} = 0$$

$$\text{or, } 4 + 0.33V_a + 0.33V_a - 3.33 - 0.33V_b = 0 \quad (1)$$

$$\text{or, } 0.66V_a - 0.33V_b = 0.67$$

$$\text{or, } 0.66V_a - 0.33V_b = 0.67 \quad (1)$$

At node b ,

$$\frac{V_b + 10 - V_a}{3} + \frac{V_b}{5} + \frac{V_b}{1} = 0$$

$$\text{or, } 0.33V_b + 3.33 - 0.33V_a + 0.2V_b + V_b = 0$$

$$\text{or, } 1.53V_b - 0.33V_a = -3.33 \quad (2)$$

$$\text{or, } 3.06V_b - 0.66V_a = -6.66 \quad (2)$$

From (1) and (2),

$$2.73V_b = -7.33$$


$$\text{or, } V_b = -2.685V; \quad V_a = -2.358V$$

Again $i = -\left(\frac{V_b}{5}\right)$. [$\because i$ shown in is against the direction of assumed respective branch ct.]

$$\text{i.e., } = -\frac{2.685}{5} = 0.537A$$

current in branch a-b is $\frac{V_a - V_b}{R} = \frac{3}{3} A = 1 A$.
 i.e. $V_2 = 3.22 \times 1 = 3.22 V$.

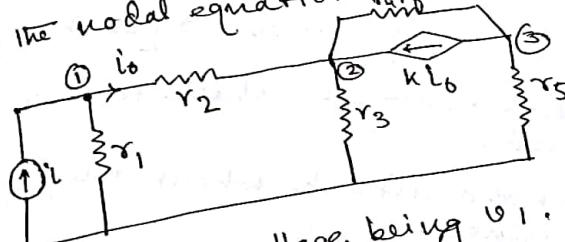Develop the nodal equation of the circuit shown in Matrix form.



Sol. At node (1), the voltage being V_1 .

$$i = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

$$\text{or, } V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \cdot \frac{1}{R_2} = i$$

$$\text{At node (2)}, K_{i_o} = \frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4} + \frac{V_2 - V_1}{R_2}$$

$$\text{or, } -\frac{V_1}{R_2} + V_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_2} \right) - V_3 \cdot \frac{1}{R_4} = K_{i_o}$$

$$\text{At node (3)}, K_{i_o} + \frac{V_3}{R_5} + \frac{V_3 - V_2}{R_4} = 0.$$

$$K_{i_o} + \frac{V_3}{R_5} + \frac{V_3 - V_2}{R_4} + K_{i_o} = 0.$$


$$\text{or, } V_3 \left(\frac{1}{R_4} + \frac{1}{R_5} \right) - V_2 \cdot \frac{1}{R_4} + K_{i_o} = -K_{i_o}$$

$$\text{or, } -V_2 \cdot \frac{1}{R_4} + V_3 \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = -2K_{i_o}$$

In Matrix form,

$$\begin{bmatrix} (1/R_1 + 1/R_2) & (-1/R_2) & 0 \\ -1/R_2 & (1/R_3 + 1/R_4 + 1/R_2) & (-1/R_4) \\ 0 & -1/R_4 & (1/R_4 + 1/R_5) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} i \\ K_{i_o} \\ -K_{i_o} \end{bmatrix}.$$

Node and Mesh Analysis :

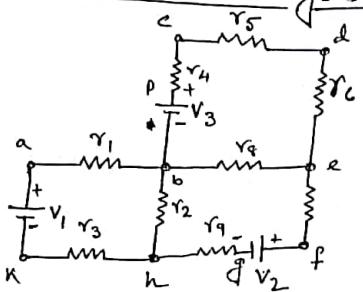

No. of Circuit elements = 12
[9 resistors + 3 voltages]

No. of Nodes = 10 [a, b, c, d, e, f, g, h, i, j]

No. of junction points = 3

No. of branches = 5 [bade, be, bh, bi, ej]

No. of meshes = 3 [abhe, bde, bhj]

Node : It is an equipotential point at which two or more elements are joined.

Junction : It is that point of a network where three or more elements are joined.

Branch : It is a part of a network which lies between junction points.

Circuit Element	Voltage (Volts)	Current (amps)	Power (watts).
R (Ω)	$v = Ri$	$i = \frac{v}{R}$	$p = i^2 R$.
L (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} [v dt + i_0]$ [i_0 being initial current].	$p = L i \frac{di}{dt}$
C (F)	$v = \frac{1}{C} \int idt + v_0$ [v_0 being initial voltage]	$i = C \frac{dv}{dt}$	$p = C v \frac{dv}{dt}$

$$C = \frac{q}{v} \text{ i.e. } i = C \frac{dv}{dt} \quad [\because i = \frac{dq}{dt}]$$

$$\text{or, } dv = \frac{1}{C} idt$$

$$\text{or, } \int_{v_0}^{v_f} dv = \frac{1}{C} \int_0^t idt. \quad [v_0 \text{ initial voltage of capacitor, } v_f = \text{final voltage of capacitor}]$$

$$\text{or, } v_f - v_0 = \frac{1}{C} \int_0^t idt.$$

$$\text{i.e. } v_f = \frac{1}{C} \int_0^t idt + v_0.$$


The power absorbed by the capacitor is given by

$$p = v i = v C \frac{dv}{dt}.$$

Energy stored by the capacitor is

$$W = \int_0^t p dt = \int_0^t v C \frac{dv}{dt} dt = \frac{1}{2} C v^2.$$

Problem
Determine cur-

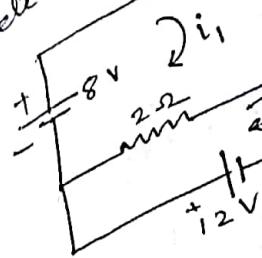

for loop 1
 $20(i_1 - i_2)$

or, $2A - 2i_1 - 2i_2$

for loop 2
 $20(i_2 - i_1)$

or, $-20i_1$

for loop 3
 $2(i_3 - i_1)$


or, $2i_3 - 2i_1$

∴

ig

Problem

Determine current in 5Ω resistor

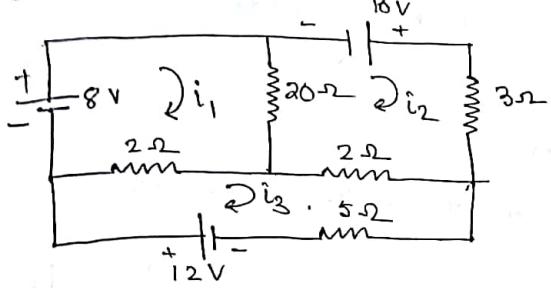

For loop 1

$$20(i_1 - i_2) + 2(i_1 - i_3) = 8 \text{ V}$$

or, $22i_1 - 20i_2 - 2i_3 = 8$

For loop 2

$$20(i_2 - i_1) + 3i_2 + 2(i_2 - i_3) = 10$$

or, $-20i_1 + 25i_2 - 2i_3 = 10$

For loop 3

$$2(i_3 - i_1) + 2(i_3 - i_2) + 5i_3 = 12$$

or, $-2i_1 - 2i_2 + 9i_3 = 12$

$$\therefore \begin{bmatrix} 22 & -20 & -2 \\ -20 & 25 & -2 \\ -2 & -2 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 10 \\ 12 \end{bmatrix}$$

$$i_3 = \frac{\begin{vmatrix} 22 & -20 & 8 \\ -20 & 25 & -10 \\ -2 & -2 & 12 \end{vmatrix}}{\begin{vmatrix} 22 & -20 & -2 \\ -20 & 25 & -2 \\ -2 & -2 & 9 \end{vmatrix}} = \frac{22(300 - 20) + 20(-240 - 20)}{22(225 - 4) + 20(-180 - 4) - 2(40 + 50)}$$

$$= \frac{6160 + (-5200) + 720}{4862 + (-3680) - 180}$$

$$= \frac{1680}{1002} \approx 1.67 \text{ Amp}$$


Millman's Theorem for AC Network:

As per Millman's Theorem:

$$V_m = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3 + \dots + V_n Y_n}{Y_1 + Y_2 + \dots + Y_n}$$

$$\text{and } Z_m = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$$

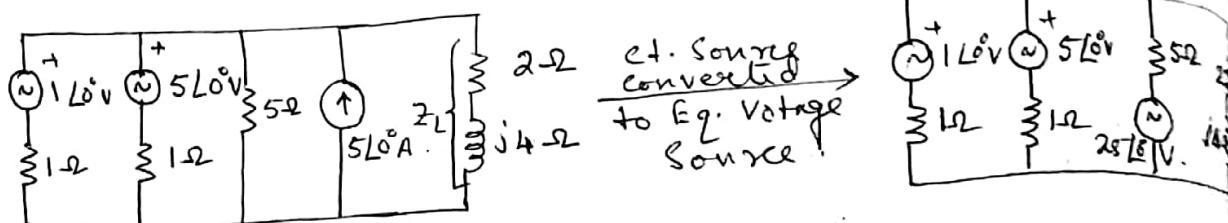Using Millman's Theorem find the circuit in the Load Z_L .



Equivalent Voltage source is given by,


$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$= \frac{1 L0^\circ \times 1/1 + 5 L0^\circ \times 1/1 + 25 L0^\circ \times 1/5}{1/1 + 1/1 + 1/5}$$

$$= \frac{11}{2.2} = 5 L0^\circ V.$$

$$\therefore I_L = \frac{E}{Z_L} = \frac{5 L0^\circ}{2 + j4} = 1.12 L - 63.43^\circ A.$$

Fig. represent a steady state circuit in s-domain.
Find its Thevenin's Equivalent at the right of terminal x-y.

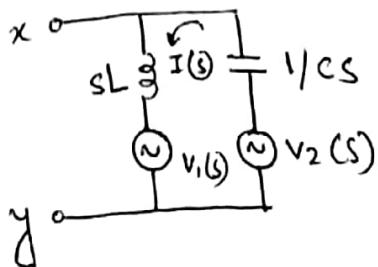



Let $I(s)$ be the circulating loop current as shown.
Obviously, $I(s) = \frac{v_2(s) - v_1(s)}{sL + 1/cs}$.

Assuming the open circuit voltage across x-y terminal to be $V_{o.c.}$, application of KVL gives.

$$\begin{aligned} V_{o.c.} &= sL I(s) + v_1(s) \\ &= v_1(s) + sL \frac{v_2(s) - v_1(s)}{sL + 1/cs} \\ &= \frac{v_1(s) + s^2 L c v_2(s)}{s^2 L c + 1} \end{aligned}$$

With independent sources deactivated, the internal impedance,
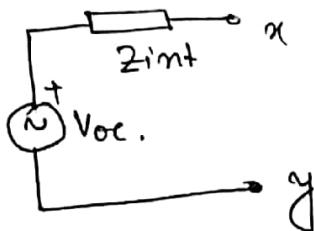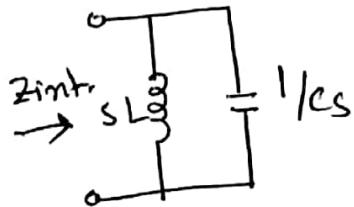
$$Z_{int} = sL \parallel \frac{1}{cs} = \frac{sL(1/cs)}{sL + 1/cs} = \frac{sL}{s^2 L c + 1}$$



THEVENIN'S THEOREM

Nabanita Chatterjee
(EE Dept)

It is possibly the most extensively used network theorem. It is applicable where it is desired to determine the current through or voltage across any one element in a network without going through the rigorous method of solving a set of network equations.

It provides a mathematical technique for replacing a given network, as viewed from two output terminals, by a single voltage source with a series resistance. It makes the solution of complicated networks quite quick and easy.

Statement :


Any two terminal bilateral linear d.c. circuits can be replaced by an equivalent circuit consisting of a voltage source and a series resistor.

The Thevenin voltage v is the open circuit voltage at terminals A and B.


The Thevenin resistance is the resistance seen at AB with all voltage sources replaced by short circuits and all current sources replaced by open circuits.

Explanation

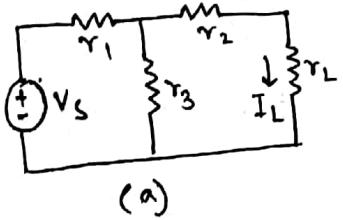Let us consider a simple d.c. circuit shown in Fig (a). We are to find I_L by Thevenin's Theorem. In order to find the equivalent voltage source, r_L is removed [Fig (b)] and $V_{o.c.}$ is calculated.



(a)

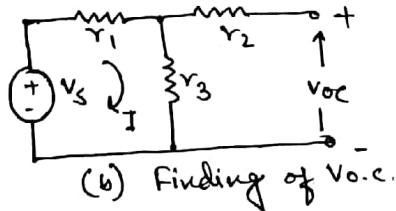


(b) Finding of $V_{o.c.}$

$$V_{o.c.} = I r_3 = \frac{V_s}{r_1 + r_3} \cdot r_3$$

A more general statement of Thevenin's theorem is that any linear active network consisting of independent and/or dependent voltage and current sources and linear bilateral network elements can be replaced by an equivalent circuit consisting of a voltage source in series with a resistance, the voltage source being the open circuited voltage across the open circuited load terminals and the resistance being the internal resistance of the source network looking through the open circuited load terminals.

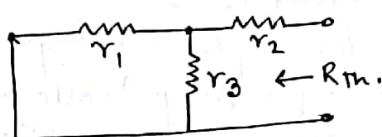Next, to find the internal resistance of the network (Thévenin's e. or equivalent resistance) in series with $V_{o.c.}$, the source is removed (deactivated) by a short circuit (as source does not have any internal resistance) as shown fig. (c).




$$R_{Th} = r_2 + \frac{r_1 \cdot r_3}{r_1 + r_3}$$

(c). Finding of R_{Th} .

As per Thévenin's theorem, the equivalent circuit being

Fig. (d)

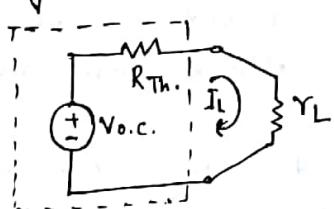

$$I_L = \frac{V_{o.c.}}{R_{Th} + R_L} \text{ Ampere.}$$

Fig. (d) Finding of I_L .

Steps for Solution of a Network Utilizing Thévenin's Theorem :

Step 1: Remove the load resistor (R_L) and find the open circuit voltage ($V_{o.c.}$) across the open circuited load terminals.

Step 2: Deactivate the constant sources (for voltage source, remove it by internal resistance and for current source delete the source by open circuit) and find the internal resistance (Thévenin's Resistance) of the source side looking through the open circuited load terminals. Let this resistance be R_{Th} .

Step 3: Obtain Thévenin's equivalent circuit by placing R_{Th} in series with $V_{o.c.}$.

Step 4: Reconnect R_L across the load terminals as shown.



Equivalent Source.

Thévenin's Equivalent Network

Obviously I (the load current)
 $= \frac{V_{o.c.}}{R_{Th} + R_L}$

Thevenin's equivalent voltage (as shown) = $\frac{V_{oc}}{R_{Th}}$
 Thevenin's Equivalent resistance or Internal impedance

Different Methods of Finding R_{Th}

for Independent Sources:

The most common method of finding R_{Th} , the internal resistance of any linear, bilateral network containing independent current or voltage sources is to deactivate the source by internal resistance i.e. for independent current source, deactivate it by removing the source and for voltage source, deactivate it by shorting it (assuming internal resistance of the voltage source being zero). Then find the internal resistance of the network looking through the load terminals kept open circuited.

(b). For circuit containing dependent sources in addition to or in absence of independent source

1st Method:

Find V_{oc} across the open circuited load terminals by conventional network analysis. Next, short the load terminals and find the short circuit current (I_{sc}) through the shorted terminals.

The internal resistance of the source network is then obtained as

$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

2nd Method:

Remove the load resistance and apply a d.c. deriving voltage V_{dc} at the open circuited load terminals. Keep the other independent sources deactivated during this time (i.e. short the voltage source terminals and open the current source terminals). A d.c. deriving current i_{dc} will flow in the circuit from the load terminals due to application of V_{dc} .

The internal resistance of the source network is then obtained as

$$R_{Th} = \frac{V_{dc}}{i_{dc}}$$


X

$$= \frac{r_1 r_2 r_3 + r_1 r_2 r_4 + r_3 r_4 r_1 + r_3 r_4 r_2}{(r_1 + r_4)(r_3 + r_2)}$$

\therefore In the given bridge circuit,

$$V_{o.c} = \frac{E(r_1 r_2 - r_3 r_4)}{(r_1 + r_2)(r_3 + r_4)} \text{ and } R_{int} = \frac{r_1 r_2 r_3 + r_1 r_2 r_4 + r_3 r_4 r_1 + r_3 r_4 r_2}{(r_1 + r_2)(r_3 + r_4)}$$

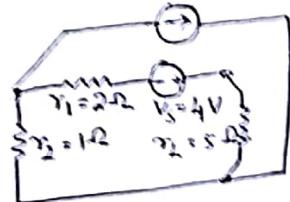
- ③ In the circuit find the power loss in r_L .



Removal.

I_o

r_L

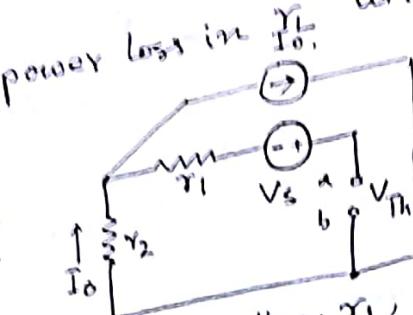



V_{Th} \Rightarrow open ckt. across open load terminals

$$\text{Here } V_{Th} = V_s - I_o r_2 \quad [\because \text{no ct. flows thru } r_1, \text{ no voltage drop across } r_1]$$

$$\text{or, } V_{Th} = 4 - 2 \times 1 = 2 \text{ V.}$$

To find R_{int} (i.e. internal resistance of the ckt. across a-b), all com. sources are deactivated i.e. $V_s = 0$ and $I_o = 0$.
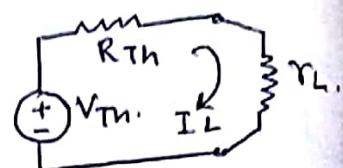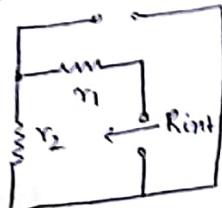
$$\text{Obviously } R_{Th} = r_1 + r_2 = 3 \Omega$$




Thus we have obtained the equivalent Thvenin's circuit when

$$V_{o.c} = V_{Th} = 2 \text{ V, } R_{Th} = R_{int} = 3 \Omega.$$

$$\therefore I_L \text{ (load current through } r_L) = \frac{2}{3 + r_L} = \frac{2}{3 + 8} = \frac{1}{5} \text{ A} = 0.25 \text{ A.}$$

$$\therefore \text{Power Loss } P_L \text{ in } r_L = I_L^2 \times r_L = (0.25)^2 \times 5 = 0.3125 \text{ Watt.}$$

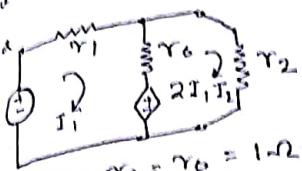Find the Thvenin's equivalent circuit for the network shown at the right of terminal a-b.



$$b) \eta = r_2 = r_0 = 1\Omega$$

Let the terminals a-b be open circuited. This leads to $I_1 = 0$ and the depending voltage source $2I_1$ is also zero. Also $I_2 = 0$. Obviously V_{oc} is zero.

Next, a dc voltage supply V_{dc} be applied across a-b such that the input current be I_1 at terminal a.

Applying KVL at the left loop under this condition,

$$\text{Applying KVL at the left loop under this condition,}$$

$$V_{dc} = I_1 r_1 + I_1 r_0 - I_2 r_0 + 2I_1 \quad \dots \text{(a)}$$

$$\text{or, } V_{dc} = r_1 I_1 + r_0 (I_1 - I_2) + 2I_1 \quad \dots \text{(b)}$$

$$\text{Applying KVL at the outer loop, } V_{dc} = r_1 I_1 + r_2 I_2 \quad \dots \text{(c)}$$

$$\text{However } r_1 = r_2 = r_0 = 1\Omega \Rightarrow V_{dc} = 4I_1 - I_2 \quad \dots \text{(c')}$$

$$\therefore \text{(a) becomes } V_{dc} = I_1 + I_1 - I_2 + 2I_1 \Rightarrow V_{dc} = 4I_1 - I_2 \quad \dots \text{(d)}$$

$$\text{and (b) becomes } V_{dc} = I_1 + I_2 \quad \dots \text{(d')}$$

$$\text{from (d) } I_2 = V_{dc} - I_1 \quad \dots \text{(d'')}$$

$$\text{Using this value of } I_2 \text{ in (c'), } V_{dc} = 4I_1 - (V_{dc} - I_1)$$

$$\text{or, } 2V_{dc} = 5I_1$$


$$\therefore \frac{V_{dc}}{I_1} = \frac{5}{2} = 2.5\Omega$$

Thus the internal resistance of the circuit across a-b is 2.5Ω .

The given circuit is thus modified to give

$$V_{oc} = 0V, R_{int} = 2.5\Omega$$

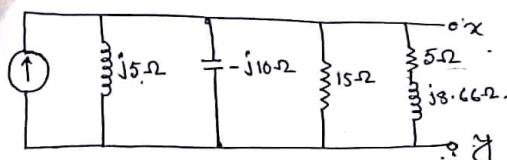5. If $I = 33L - 13^\circ A$, find the Thvenin's Equivalent circuit to the terminals $x-y$ in the network.



Sol. Let us first find the equivalent impedance across the current. However, assuming the equivalent admittance to be Y_{eq} , we get that,

$$Y_{eq} = Y_1 + Y_2 + Y_3 + Y_4$$

$$Y_1 = \frac{1}{j5} = -j0.2 \text{ mho}, \quad Y_2 = \frac{1}{-j10} = j0.1 \text{ mho}$$

$$Y_3 = \frac{1}{15} = 0.067 \text{ mho}, \quad Y_4 = \frac{1}{5+j8.66} = \frac{1}{16.66} = (0.05 - j0.0866) \text{ mho}$$

$$\therefore Y_{eq} = (0.117 - j0.1866) \text{ mho.}$$

$$\text{Then, } V_{x-y} = (V_{oc}) = I/Y_{eq} = 33L - 13^\circ / (0.117 - j0.1866) = 150L45^\circ \text{ V.}$$

To find $Z_{in} (= Z_{Th})$, the current source is deactivated and by inspection it is observed that

$$Z_{in} = \frac{1}{Y_{eq}} = \frac{1}{0.117 - j0.1866} = \frac{1}{0.22L58^\circ} = 4.545L58^\circ$$


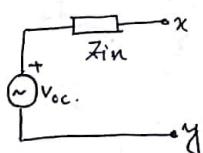


Fig (a) Thvenin's Equivalent Circuit

$$Z_{in} = 4.545L58^\circ \Omega \text{ and}$$

$$V_{oc} = 150L45^\circ \text{ V.}$$

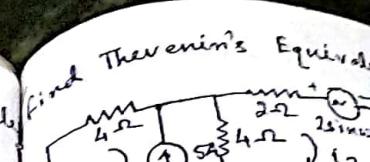

$$\text{In loop 1: } (4+4)i_1 - 8i_1 -$$

$$\text{In loop 2: } i_2(4+4) - 8i_2 -$$

$$\text{or, } -4i_1 -$$

$$\text{or, } -2i_1 -$$

$$8i_1 = 4$$

$$\text{from (1), } 8i_1 = 4$$

using the value

$$-2(0.5i_2 - 1)$$

$$\text{or, } -i_2 + 3.5$$


$$\text{or, } 4i_2 = 6.5$$

$$\text{or, } i_2 = 1.625$$

$$\therefore V_{oc} = 6.25$$


$$V_{oc} = 6.0$$

To find the R_{in} replaced by the

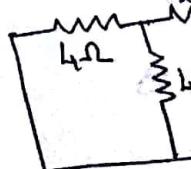


$$R_{in} =$$

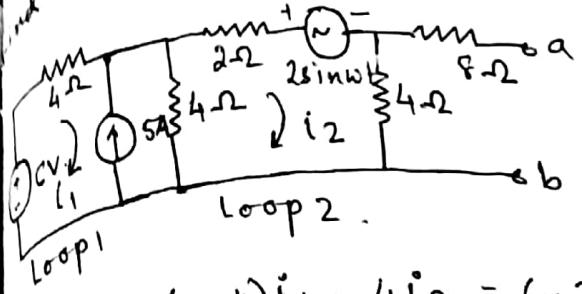Find Thevenin's Equivalent Circuit of the network shown:



\Rightarrow

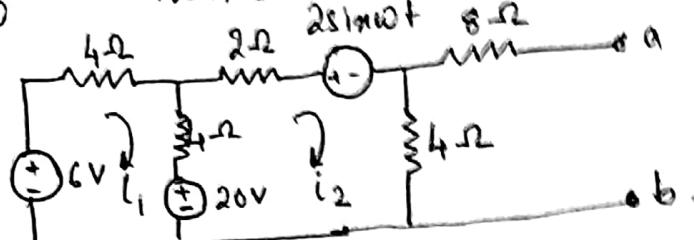

$$\text{Loop 1: } (4+4)i_1 - 4i_2 = 6 - 20 \\ 8i_1 - 4i_2 = -14 \quad \dots \dots (1)$$

$$\text{Loop 2: } i_2(4+4+2) - 4i_2 = 20 - 2\sin\omega t$$

$$\text{or, } -4i_1 + 10i_2 = 20 - 2\sin\omega t$$

$$\text{or, } -2i_1 + 5i_2 = 10 - \sin\omega t. \quad \dots \dots (2).$$

$$\text{from (1), } 8i_1 = 4i_2 - 14 \\ \text{or, } i_1 = 0.5i_2 - 1.75 \quad \dots \dots (3).$$

Using the value of i_1 from (3) in (2)

$$-2(0.5i_2 - 1.75) + 5i_2 = 10 - \sin\omega t$$

$$\text{or, } -i_2 + 3.5 + 5i_2 = 10 - \sin\omega t.$$

$$\text{or, } 4i_2 = 6.5 - \sin\omega t$$


$$\text{or, } 4i_2 = 6.5 - 0.25 \sin\omega t.$$

$$\therefore i_2 = 1.625 - 0.25 \sin\omega t. \quad i_2 \times 4 = \frac{V_{a-b}}{(1.625 - 0.25 \sin\omega t)} 4.$$

$$\therefore V_{oc} = 6.5 - \sin\omega t.$$

$$V_{oc} = 6.5 - \sin\omega t.$$

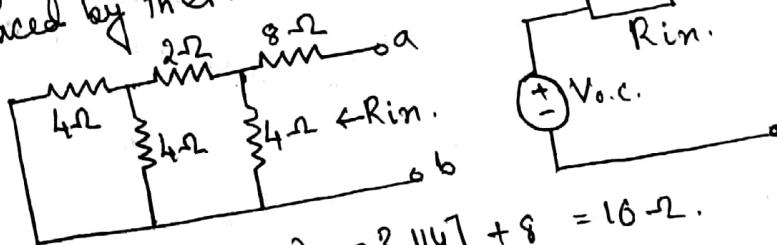To find the Thevenin's internal resistance, the sources are replaced by their internal resistances.






$$R_{in} = 10\Omega$$

$$V_{oc} = (6.5 - \sin\omega t) \Omega$$

$$R_{in} = [\{ (4||4) + 2 \} || 4] + 8 = 10\Omega.$$

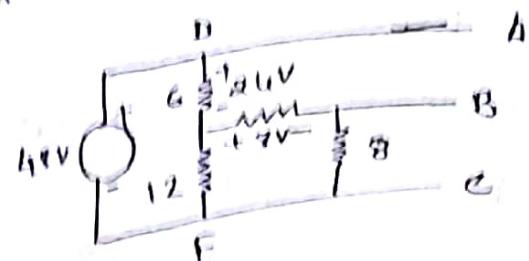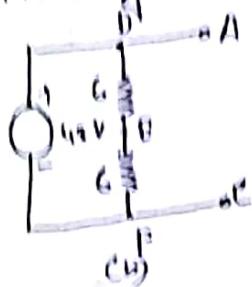
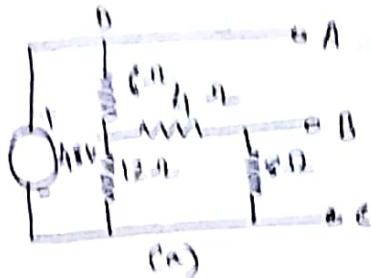
7. Calculate the value of V_{EF} and R_{EF} between terminals A and B in the circuit shown in Fig.




For getting about the terminal B for the time being those parallel paths between B and F: one consisting of 12Ω , the other of $(1+8) = 12\Omega$. Hence $R_{BF} = 12/(12 + 6) \Omega$. The source voltage of $48V$ drops across two 6Ω resistance connected in series. Hence $V_{EF} = 24V$. The same $24V$ across 12Ω resistor connected directly between E and F gives a series-connected resistance of 4Ω and 6Ω connected across E and F. Drop across 4Ω resistance $= 24 \times 4/(4+6) = 8V$ (Fig. c).

Now as we go from B to A via point E, there is rise in voltage of $8V$ followed by another rise in voltage of $24V$ thereby giving a total voltage drop of $32V$. Hence $V_{EA} = 32V$ with point A positive.

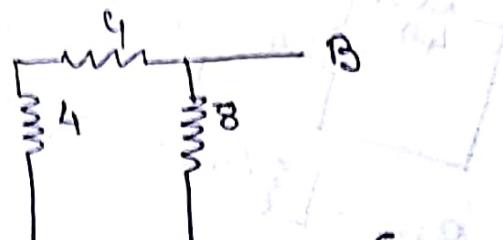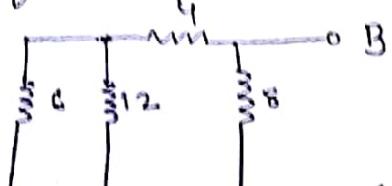For finding R_{EF} , we short-circuit the $48V$ source. This short-circuiting, in effect, combines the points A, D and F electrically as shown in (d) as seen from (a).



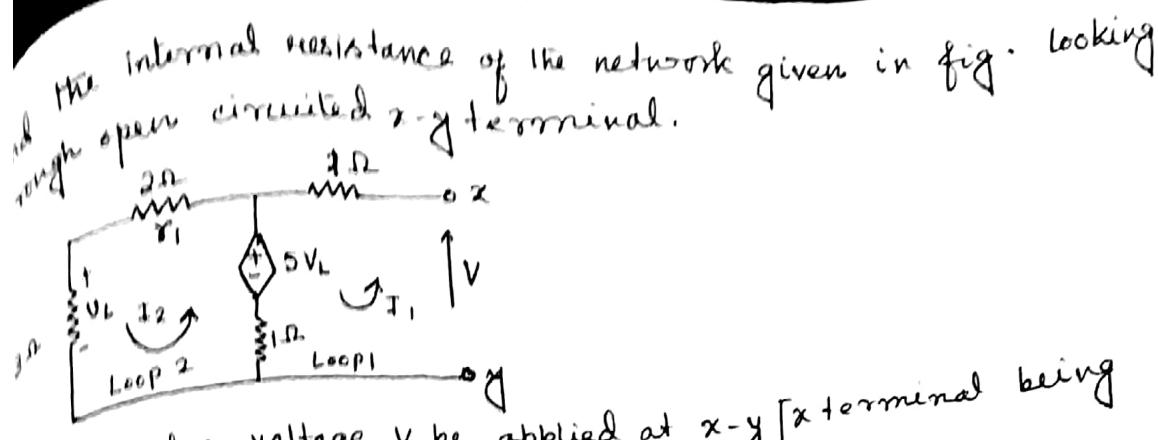

Let a d.c. voltage V be applied at x-y [x-terminal being $+V_0$]. Obviously, V_L is $(I_2 \times 3)$ or $3I_2$.

The magnitude of the dependent source is then

$$\therefore 5V_L \text{ or } (15 \times I_2) V.$$

Applying KVL in Loop-1,

$$V = (1+1)I_1 - 5V_L - 1 \times I_2$$

$$V = 2I_1 + 15I_2 - I_2 \\ = 2I_1 + 14I_2 \quad \dots \dots (1)$$

Applying KVL in Loop-2,

$$0 = (1+3+2)I_2 - 5V_L - 1 \times I_1$$

$$0 = 6I_2 - 15I_2 - I_1 \\ = -9I_2 - I_1 \quad \dots \dots (2)$$

$$\text{Thus, from (2), } I_2 = -\frac{1}{9}I_1$$

$$\therefore V = 2I_1 - 1.56I_1 \quad \dots \dots (3)$$

$$\text{obviously, from (3), } \frac{V}{I_1} = R_{int} = 0.44\Omega.$$

$$2I_1 - 16I_2 = V$$

$$-I_1 + 21I_2 = 0$$


$$I_1 = 21I_2 \\ \text{or, } I_2 = \frac{I_1}{21}, \frac{I_1}{21}$$

$$\therefore V = 2I_1 - \frac{16 \times I_1}{21} \\ = I_1 \left(2 - \frac{16}{21} \right).$$

$$= 1.2381I_1$$

$$\text{or, } \frac{V}{I_1} = 1.2381\Omega.$$

Obtain circuit.

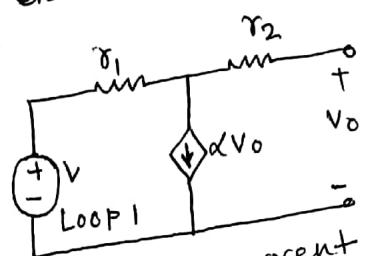

In fig., the loop current being αV_0 across r_1 ,

of $(r_1 \alpha V_0)$

Assuming $V_0 \equiv V_{o.c.}$

Application of KVL in Loop-1 gives.

$$-V_1 + r_1 \alpha V_{o.c.} + V_{o.c.} = 0$$

$$\text{or, } V_{o.c.} = V_1 - r_1 \alpha V_{o.c.}$$

$$\text{i.e. } V_{o.c.} (1 + r_1 \alpha) = V$$

$$\therefore V_{o.c.} = \frac{V}{1 + r_1 \alpha}$$

Thevenin's Equivalent to the left of terminal a-b in the



To determine R_{int} , a-b terminals are shorted. V_o becomes zero. Since $V_o=0$, the voltage control current source is also equal to zero. Thus r_1, r_2 are in series with V_o . All circulating current being, i.e.,

$I_{sc} = \frac{V}{r_1 + r_2}$ and hence, the internal resistance of the given network is given by

$$R_{int} = \frac{V_{o.c}}{I_{sc.c}} = \frac{V}{1+\alpha r_1} \cdot \frac{r_1 + r_2}{V} = \frac{r_1 + r_2}{1+\alpha r_1}$$

This gives the Thevenin's equivalent circuit as

$$V_{o.c} = \frac{V}{1+\alpha r_1}; R_{int} = \frac{r_1 + r_2}{1+\alpha r_1}$$

Reciprocity Theorem
shows the application

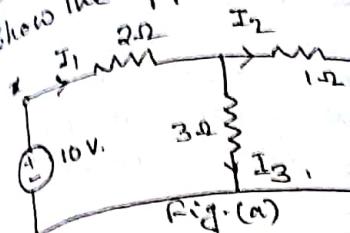


Fig.(a)

$$\therefore I_1 = \frac{10}{3.5} = 2.86$$

$$I_3 = 2.86 -$$

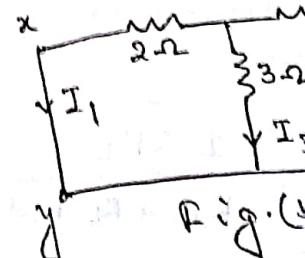


Fig.(b)

This gives,

Hence we can say, the a.c. source becomes 1.

- In any linear circuit, if any branch is shorted, then the same produce the same effect.

Reciprocity Theorem Problem

Show the application of reciprocity theorem in the network.

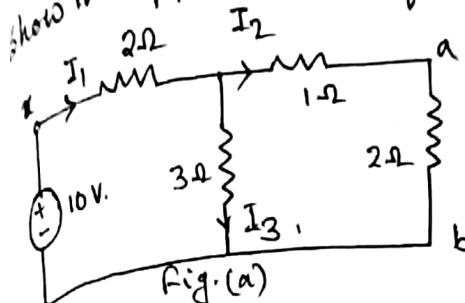


Fig.(a)

The equivalent resistance across $x-y$ is given by
 $R_{eq} = [(2+1)/1] + 2 = 3.5 \Omega$.

$$\therefore I_1 = \frac{10}{3.5} = 2.86 \text{ A}, \quad I_2 = 2.86 \times \frac{3}{3+3} = 1.43 \text{ A}.$$

$$I_3 = 2.86 - 1.43 = 1.43 \text{ A}.$$

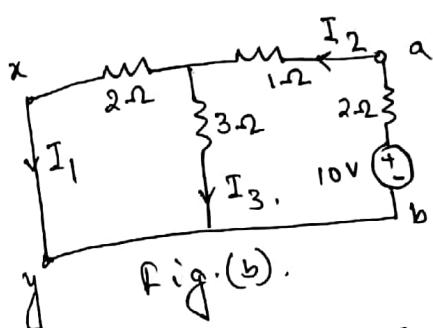


Fig.(b).

With ref to fig.(b).

Req across $x-y$ terminal

$$R_{eq} = (2/1) + 1 + 2 = 4.2 \Omega.$$

$$I_2 = \frac{10}{4.2} = 2.381 \text{ A}.$$

$$\text{This gives, } I_1 = I_2 \frac{3}{3+2} = 2.381 \times \frac{3}{5} = 1.43 \text{ A}.$$

Hence we observe that when the source was in branch $x-y$, the $a-b$ branch current is 1.43 A , again when the source is in branch $a-b$, the $x-y$ branch current becomes 1.43 A .

- In any linear bilateral network if a source of emf in any branch produces a current I in any other branch, then the same emf E acting in the second branch would produce the same current I in the first branch.

In other words, it simply means that E and I are mutually transferrable. The ratio E/I known as the transfer resistance (or impedance in a.c. system).

Another way of stating the above is that the receiving point and the sending point in a nw are interchangeable.

It also means that interchange of an ideal voltage source and an ideal ammeter in any nw will not change the ammeter reading.


Compensation Theorem

In a linear time-invariant n/w when the resistance (R) in an uncoupled branch carrying a current (I) is changed (ΔR), the currents in all the branches would change and be obtained by assuming that an ideal voltage source has been connected in series with $(R + \Delta R)$ when all other resistances in the n/w are replaced by their internal resistances.

$$I = \frac{V_0}{R_{Th} + R_L}, I' = \frac{V_0}{R_{Th} + R_L + \Delta R_L}$$

$$\begin{aligned} \Delta I &= I' - I \\ &= \frac{V_0}{R_{Th} + R_L + \Delta R_L} - \frac{V_0}{R_{Th} + R_L} \\ &= \frac{V_0 [R_{Th} + R_L - R_{Th} - R_L - \Delta R_L]}{(R_{Th} + R_L + \Delta R_L)(R_{Th} + R_L)} \end{aligned}$$

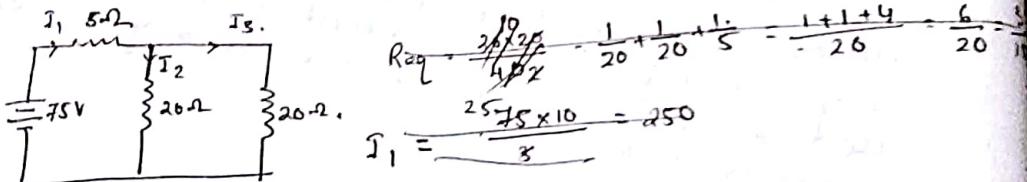
$$\begin{aligned} &= -\left(\frac{V_0}{R_{Th} + R_L}\right) \frac{\Delta R_L}{R_{Th} + R_L + \Delta R_L} = -\frac{I \Delta R_L}{R_{Th} + R_L + \Delta R_L} \\ &= -\frac{-V_L}{R_{Th} + R_L + \Delta R_L} \end{aligned}$$



$$R_{eq} = \frac{20 \times 2}{20 + 2} = \frac{1}{20} + \frac{1}{20} + \frac{1}{5} = \frac{1+1+4}{20} = \frac{6}{20}$$

$$I_1 = \frac{25 - 75 \times 10}{3} = 250$$

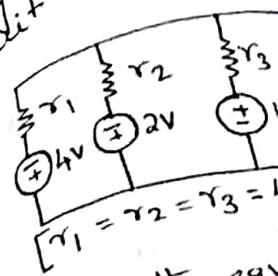Using Millman's theorem
in circuit and find H



Let V be the eq resistance to be of the Millman

$$V = -$$

$$\text{and } R = \frac{1}{G}$$

Substitution

$$V = -$$


$$\text{and } R = \frac{1}{G}$$

When electric current flows from any resistor, there would be a voltage drop across the resistor due to Ohm's Law. This dropped voltage opposes the source voltage. Hence voltage drop across an electric resistance in any network can be assumed as a voltage source

The
the drop

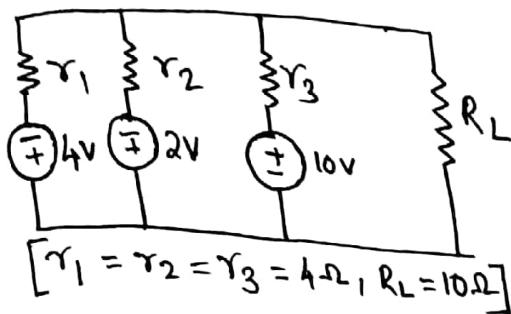Example:

Using Millman's theorem, find the current through R_L in the circuit and find the voltage drop.



Let V be the equivalent voltage source while R the equivalent resistance to be inserted in series with the voltage source of the Millman's equivalent network.

$$\text{Here, } V = \frac{-V_1 G_1 - V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3},$$


$$\text{and } R = \frac{1}{G} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}.$$

Substituting the numerical values,

$$V = \frac{-4 \times \frac{1}{4} - 2 \times \frac{1}{4} + 10 \times \frac{1}{4}}{\frac{1}{4} + \frac{1}{4} + \frac{1}{4}} = \frac{-1 - \frac{1}{2} + \frac{5}{2}}{\frac{3}{4}} = \frac{4}{3} \text{ V.}$$


$$\text{and } R = \frac{1}{\frac{1}{4} + \frac{1}{4} + \frac{1}{4}} = \frac{1}{\frac{3}{4}} = \frac{4}{3} \Omega.$$
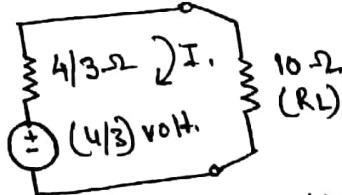
$$I = \frac{\frac{4}{3}}{\frac{4}{3} + 10} = \frac{\frac{4}{3}}{\frac{34}{3}} = \frac{4}{34} = 0.12 \text{ A.}$$



The current through 10Ω resistor is thus 0.12 A while the drop across it is $10 \times 0.12 = 1.2 \text{ V.}$

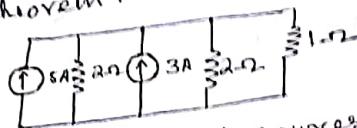2. Find the current through the $1\text{-}\Omega$ resistor using Millman's theorem.



First, the current sources are combined such that the total current is obtained as.


$$I = I_1 + I_2 = 5 + 3 = 8\text{ A.}$$

$$G = G_1 + G_2 = \frac{1}{2} + \frac{1}{2} = 1\text{ mho.}$$

converting current source to an equivalent voltage source.

$$V = \frac{I}{G} = \frac{8}{1} = 8\text{ V.}$$

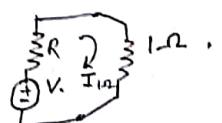
$$\text{and } R = \frac{1}{G} = 1\text{-}\Omega.$$




The current through $1\text{-}\Omega$ resistor is

$$I_{1,2} = \frac{V}{R+1} = \frac{8}{1+1} = 4\text{ A.}$$

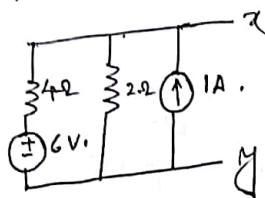3. Find the Millman's Equivalent circuit for the left of the terminal $x-y$.



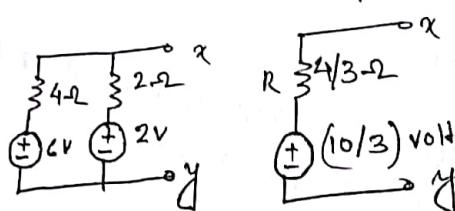Let us first convert the current source of 1A to voltage source.




Millman's Equivalent voltage is then given by

$$V = \frac{V_1 G_1 + V_2 G_2}{G_1 + G_2} = \frac{6 \times 1/4 + 2 \times 1/2}{1/4 + 1/2} = 10/3\text{ V.}$$

$$R = \frac{1}{1/4 + 1/2} = 4/3\text{ }\Omega.$$

the resulting source.

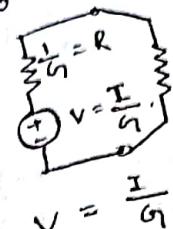

$$V = \frac{I}{G} =$$

and - sign
sources may
Also $R = \frac{1}{G}$

and $V =$

where R is the
voltage source

thus finally

steps:


Step 1 Obtain (V_1, V_2)

remove

Step 2 Apply $sources$

Step 3 Determine eqn

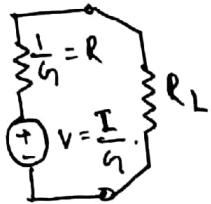+ the resulting current source is converted to an equivalent voltage source.



$$\text{thus } V = \frac{I}{G} = \frac{\pm I_1 \pm I_2 \pm I_3 \pm \dots \pm I_n}{G_1 + G_2 + G_3 + \dots + G_n}$$

[+ and - signs appeared to include the cases where the sources may not be supplying current in the same direction.]

$$\text{Also } R = \frac{1}{G} = \frac{1}{G_1 + G_2 + G_3 + \dots + G_n}$$

$$= \pm \frac{V_1}{R_1} \pm \frac{V_2}{R_2} \pm \dots \pm \frac{V_n}{R_n}$$

$$\text{and } V = \frac{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}{1}$$

where R is the equivalent resistance connected with the equivalent voltage sources in series.

$$\text{thus finally, } V = \frac{\pm V_1 G_1 \pm V_2 G_2 \pm \dots \pm V_n G_n}{G_1 + G_2 + \dots + G_n}$$

$$= \frac{\sum_{k=1}^n V_k G_k}{\sum_{k=1}^n G_k} \text{ and } G_k = \frac{1}{R_k}$$

Steps:

Step 1 obtain the conductance of each voltage source (V_1, V_2, \dots) and find G , the equivalent conductance removing the load.

Step 2 Apply Millman's theorem to find V , the equivalent voltage source.

$$V = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

Step 3 determine (R), the equivalent series resistance with the equivalent voltage source (V)

$$R = 1/G$$

Step 4 the current through the load is then given by.

$$I_L = \frac{V}{R + R_L}$$


R_L being the load resistance.

Millman's theorem:

The utility of this theorem is that, any no. of parallel sources can be reduced to one equivalent one.

Statement:

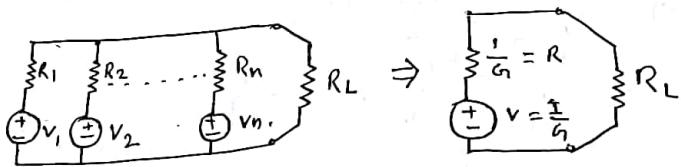When a no. of Voltage sources (V_1, V_2, \dots, V_n) are parallel having internal resistances (R_1, R_2, \dots, R_n) respectively, the arrangement can be replaced by a single equivalent voltage source V in series with an equivalent series resistance R as given below.




As per Millman's Theorem,

$$V = \frac{\pm V_1 G_1 \pm V_2 G_2 \pm \dots \pm V_n G_n}{G_1 + G_2 + \dots + G_n}$$

$$R = \frac{1}{G} = \frac{1}{G_1 + G_2 + \dots + G_n}$$

Explanation:

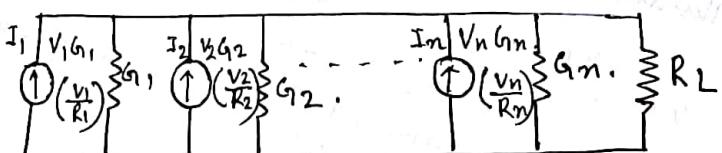Assuming a dc network of numerous parallel voltage sources with internal resistances supplying power to a load resistance R_L , all voltage sources are converted to current sources.



Let I represent the resultant current of the parallel current sources while G the equivalent conductance such that,

$$I = I_1 + I_2 + I_3 + \dots ; \quad G = G_1 + G_2 + G_3 + \dots$$




Compensation Th.

In a linear time invariant n/w, if when the impedance / resistance of a uncoupled branch carrying a ct. I is changed by ΔZ , the cts. in all the branches would change and can be obtained by assuming that an ideal voltage source of V_c (say) has been connected in series with $(Z + \Delta Z)$ when all other sources in the n/w. are replaced by the internal resistance.




$$I = \frac{V_o}{Z_{th} + Z_L}$$
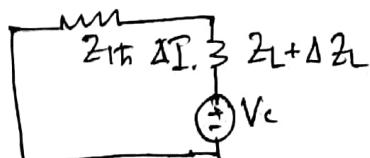
$$I' = \frac{V_o}{Z_{th} + (Z_L + \Delta Z)}$$




$$\begin{aligned} \Delta I &= I' - I = \frac{V_o(Z_{th} + Z_L - Z_{th} - Z_L - \Delta Z)}{(Z_{th} + Z_L)(Z_{th} + Z_L + \Delta Z)} \\ &= \frac{-V_o \Delta Z}{(Z_{th} + Z_L)(Z_{th} + Z_L + \Delta Z)} = \frac{-I \Delta Z}{(Z_{th} + Z_L + \Delta Z)}. \end{aligned}$$

\rightarrow compensating voltage.

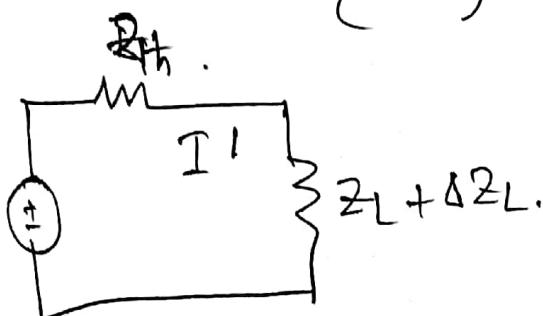


$$I' = I_1 + \Delta I.$$

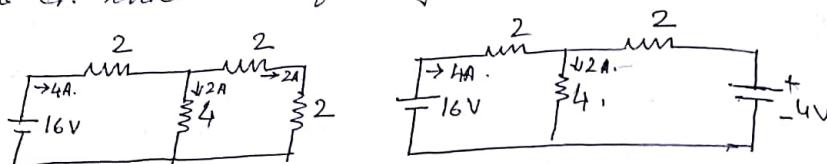According to this theorem any resistance in any branch of a network may be replaced by a voltage source that has zero internal resistance and a voltage equal to the voltage drop across the replaced resistance due to the ct. which was flowing through it.



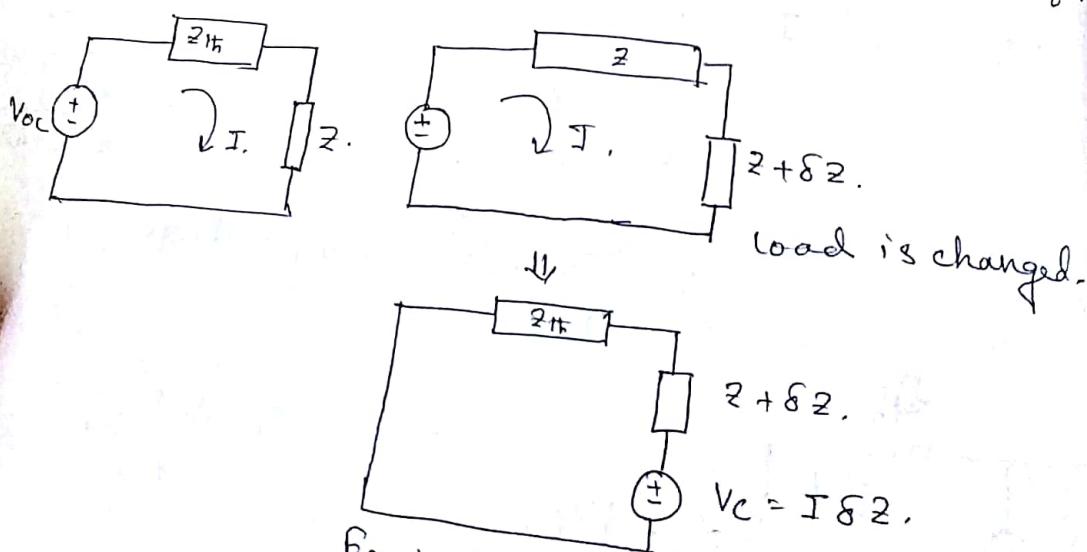In a linear network N , if the current in a branch is I and the impedance z of the branch is increased by δz , then the increment of voltage and ct. in each branch of the netw is that voltage or current that would be produced by an opposing voltage source of value $V_c = (I\delta z)$ introduced into the altered branch after the modification.



Equivalent Circuit by the compensation theorem.

Using the superposition principle
 $V_c(+)$. Assume $i(+) = e^{-4t}$; $V_c(-)$
 $i(-) = 0$

Deactivating $i(+)$

$$V_c'(s) = \frac{1}{1/R_2} \cdot \frac{1}{1/(R_2 + s)}$$

$$V_c'(+)= \pi^{-1} V_c'(s)$$

$$\text{setting } V(+) = 0.$$



$$V_c''(s) = \left(\frac{1}{1/(R_2 + s)}\right)^{-1} = \frac{s}{1+s}$$

$$V_c''(+)= [1]$$

Hence the can be written


$$V_c(+) =$$

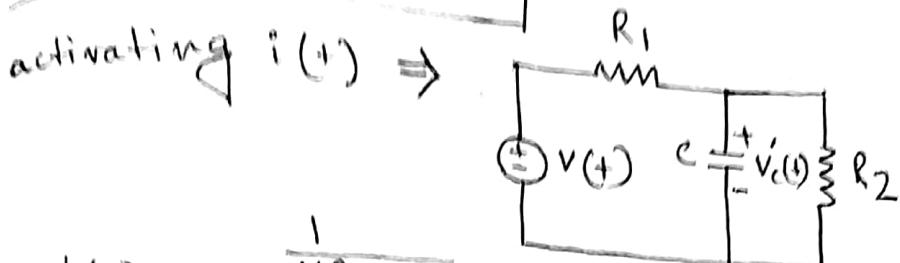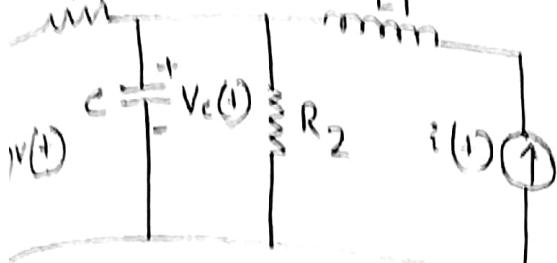using the superposition theorem calculate the voltage $v_c(+)$. Assume $R_1 = R_2 = 2\Omega$, $C = 0.5 F$, $L = 1H$, $v(+) = 5$, $i(+) = e^{-4t}$; $v_c(0) = 0$, $i_L(0) = 0$.



$$v_c'(s) = \frac{\frac{1}{1/R_2 + sC}}{\frac{1}{1/R_2 + sC} + R_1} \times v(s) = \frac{v(s)}{(s+2)} = \frac{1}{s^2 + (s+2)}$$
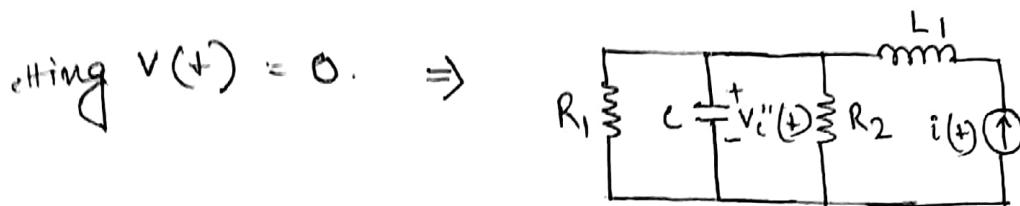
$$v_c'(+) = \mathcal{L}^{-1} v_c'(s) = \left(\frac{5}{2} + \frac{1}{4} e^{-2t} - \frac{1}{4}\right) u(+).$$





$$\begin{aligned} v_c''(s) &= \left(\frac{1}{1/R_1 + 1/R_2 + 1/sC} \right) i(s) \\ &= \left(\frac{2}{s+2} \right) \left(\frac{1}{s+4} \right) = \frac{1}{s+2} - \frac{1}{s+4} \end{aligned}$$

$$v_c''(+) = \mathcal{L}^{-1} v_c''(s) = (e^{-2t} - e^{-4t}) u(+).$$

Hence the total response due to both the sources can be written as.

$$v_c(+) = v_c'(+) + v_c''(+) = \left(\frac{5}{4} e^{-2t} - e^{-4t} + \frac{5}{2} - \frac{1}{4} \right) u(+).$$


Problem on Superposition Theorem:

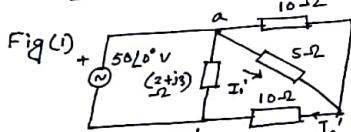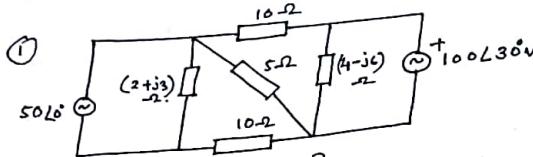

$$I_1' = \frac{50\angle 0^\circ}{(10 + 5) + 10} = 3.75\angle 0^\circ A.$$

$$I_1' = I' \frac{10}{10+5} = 2.5\angle 0^\circ A$$
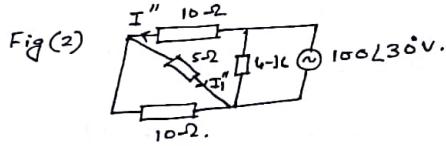
$$I'' = \frac{100\angle 30^\circ}{10 + 5 + 10} = 7.5\angle 30^\circ A.$$





$$\text{This gives } I_1'' = I'' \frac{10}{10+5} = 5\angle 30^\circ A.$$

Thus the e.t. thru 5Ω resistor, using the principle of superposition is


$$I_{5\Omega} = I_1' + I_1'' = 2.5\angle 0^\circ + 5\angle 30^\circ$$

$$= 7.273\angle 20.1^\circ A = (6.83 + j2.5)$$

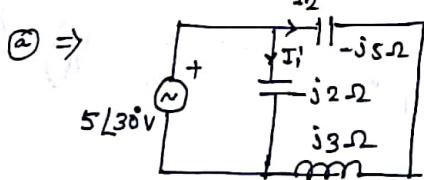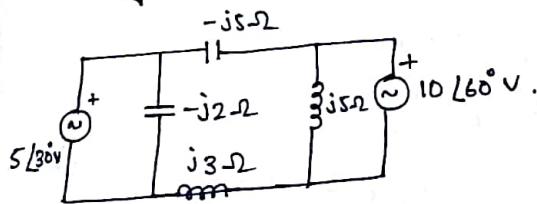- (2) Find the current through $j3\Omega$ inductive reactance using the principle of superposition.


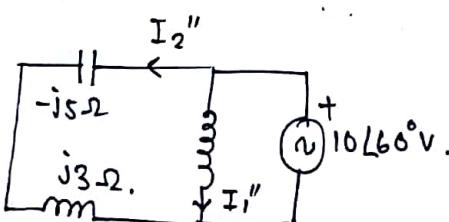
$$I_2' = \frac{5\angle 30^\circ}{-j5 + j3} = 2.5\angle 30^\circ + 90^\circ = 2.5\angle 120^\circ A.$$



$$I_2'' = \frac{10\angle 60^\circ}{-j5 + j3} = 5\angle 150^\circ A.$$

$$\begin{aligned} I_2' - I_2'' &= 2.5\angle 120^\circ - 5\angle 150^\circ \\ &= -1.25 + j2.165 + 45^\circ \\ &= -3.25 \\ &= 3.1\angle 62^\circ A. \end{aligned}$$

Mesh Analysis:
Applicable to separate
for each closed path
flow either in clockwise

Next the polarities
be find out by the

Next we can al
the loop equatio
cts. thru differ

No. of mesh e
 $m =$

Node Analysis

To compute

To write c
respective
other v o'

No. of i
 $n =$

Node:

junction:

branch:

$\cos \phi$

Mesh Analysis :

Applicable to separate closed paths of a complete ckt / R/W.

for each closed path one particular current is assumed to flow either in clockwise or in anticlockwise direction.

Next the polarities of drops across each element has to be find out by the assumed direction of current.

Next we can apply KVL for each closed loop and the loop equations has to be solved to find out different cts. thru different elements.

No. of mesh equation required to form it

$$m = b - j + 1, \quad b \Rightarrow \text{branch} \\ j \Rightarrow \text{junction}$$

Node Analysis :

To compute all the branch currents.

To write ct. expression it is assumed that the respective node potential is always higher than the other voltages appearing in the equation.

No. of independent node-pair equation needed is


$$n = j - 1, \quad j = \text{no. of junctions.}$$

Node :

junction :

branch :
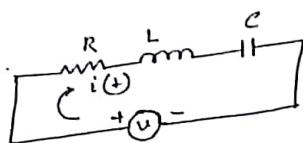
$$\cos \phi = \frac{V_R}{V_Z} = \frac{I_R}{I^2} =$$



Assuming initial condition of the current and that in capacitor the input current.

using KVL.

$$u(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt.$$

Laplace.

$$RI(s) + sLI(s) - Li(0^+) + \frac{1}{sC} I(s) + \frac{V_0}{s} = V(s).$$

$$\text{or, } RI(s) + sLI(s) - Li(0^+) + \frac{I(s)}{Cs} + \frac{Q_0}{Cs} = V(s).$$

$$\therefore I(s) \left[R + sL + \frac{1}{Cs} \right] = V(s) - \frac{Q_0}{Cs} + Li(0^+).$$

$$\Delta f = f_2 - f_1$$

The power i/p at f_1 and f_2 .



$$P = I^2 R = \left(\frac{I_{\max}}{\sqrt{2}} \right)^2 R = \frac{I_{\max}^2 R}{2} = \frac{1}{2} P_{\max}.$$

$f_1, f_2 \Rightarrow$ half power points corresponding bandwidth is termed as half-power bandwidth or -3dB bandwidth.

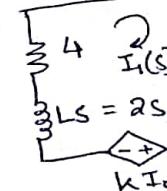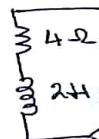1. The eff. is $I_{\max}/\sqrt{2}$.
2. Impedance is $f_2 R$ or $\sqrt{2} Z_{\min}$.
3. $P_1 = P_2 = P_{\max}/2$.
4. The eff. phase angle $\phi = \pm 45^\circ$ or $\pi/4$ rad.
5. Tangent of the eff. phase angle at the off-resonance freq. f_1 and f_2 , $Q = \tan \theta = \tan 45^\circ = 1$.

The impedance is $\sqrt{2}$ times its impedance at resonance so it is $I_{\max}/\sqrt{2}$. But the impedance at resonance $Z = R$ so at half-power points the impedance is $\sqrt{2} R$. Since $Z = \sqrt{R^2 + X^2}$, therefore, $\sqrt{2} R = \sqrt{R^2 + X^2}$ or $X = R$.

Analysis:
transform the
mesh
independent
voltage
opposite
current



In loop 1:



In loop 2:

In Ma

$\therefore I_1(s)$
given

Analysis:

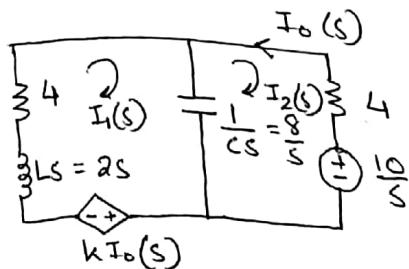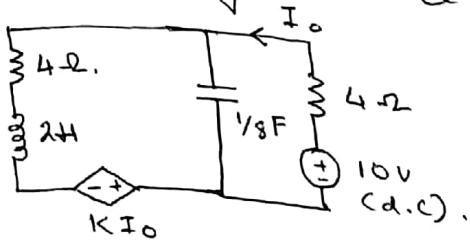Perform the circuit given in fig. to s-domain and by mesh analysis to find the current through the dependent voltage source (in s-domain).



$$\text{In loop 1: } \left(4 + 2s + \frac{8}{s}\right) I_1(s) - \frac{8}{s} I_2(s) + k I_o(s) = 0.$$

$$\text{or, } \left(4 + 2s + \frac{8}{s}\right) I_1(s) - \frac{8}{s} I_2(s) - k I_2(s) = 0 \quad [\because I_o(s) = -I_2(s)]$$

$$\text{or, } \left(4 + 2s + \frac{8}{s}\right) I_1(s) - I_2(s) \left(\frac{8}{s} + k\right) = 0.$$

$$\text{In loop 2: } 4 I_2(s) + \frac{10}{s} + I_2(s) \cdot \frac{8}{s} - I_1(s) \frac{8}{s} = 0$$

$$\text{or, } -\frac{8}{s} I_1(s) + I_2(s) \left(4 + \frac{8}{s}\right) = -\frac{10}{s}$$

In Matrix Form:


$$\begin{bmatrix} \left(4 + 2s + \frac{8}{s}\right) & -\left(\frac{8}{s} + k\right) \\ -\frac{8}{s} & \left(4 + \frac{8}{s}\right) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 0 \\ -\frac{10}{s} \end{bmatrix}$$

I₁(s), the current through the dependent source is


given by,

$$\frac{\begin{vmatrix} 0 & -\frac{8}{s} - k \\ -\frac{10}{s} & 4 + \frac{8}{s} \end{vmatrix}}{\Delta} = \frac{-10 - s \left(\frac{10}{8} k\right)}{s(s^2 + 4s + 8 - k)}$$

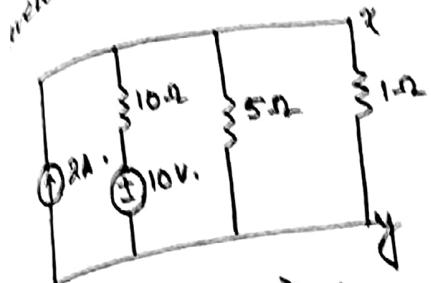In the circuit find the power loss in the 1Ω resistor by
Thevenin's Theorem.




Removing R_L (1Ω) \Rightarrow

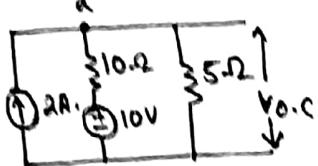

Application of KCL at Node 'a' results,


$$\frac{V_{oc}}{5} + \frac{V_{oc}-10}{10} = 2$$

$$\therefore V_{oc} = 10V.$$

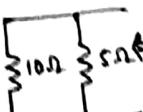To find R_{int} \Rightarrow 

$$R_{int} \text{ or } R_{Th} = \frac{5 \times 10}{5+10} = 3.33\Omega.$$


Thevenin's Equivalent Circuit.

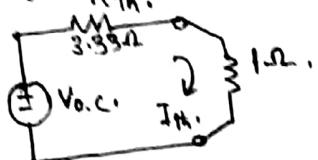

Current through 1Ω resistor is
 $I_{Th} = \frac{V_{oc}}{R_{Th} + 1} = \frac{10}{3.33 + 1} = 2.31A.$

$$\therefore \text{Power Loss in } 1\Omega \text{ resistor} = (2.31)^2 \times 1 = 5.33W.$$

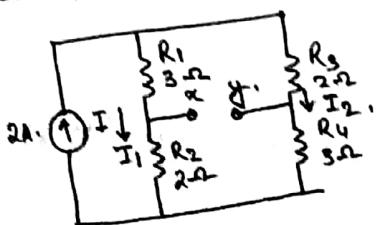For the network, find V_{x-y} and R_{int} (across x-y) using
Thevenin's Theorem.



[by current division rule].

$$I_1 = I \cdot \frac{R_3 + R_4}{(R_1 + R_2) + (R_3 + R_4)}$$

$$= 1A.$$

$$I_2 = I \times \frac{R_1 + R_2}{(R_1 + R_2) + (R_3 + R_4)} = 1A.$$

Thus voltage drop across $R_2 = 1 \times 2 = 2V.$
voltage drop across $R_4 = 1 \times 3 = 3V.$


$$\therefore V_{x-y} = V_x - V_y = 2V - 3V = -1V.$$

i.e. Y is at higher potential.


To find R_{int} across x-y, current source is removed and $(R_1 + R_2)$ is in parallel to $(R_3 + R_4)$.

$$(R_1 + R_2) \parallel (R_3 + R_4) = 5/15 = 2.5\Omega.$$

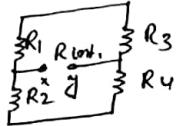
$$\therefore R_{int} = (R_1 + R_2) \parallel (R_3 + R_4).$$



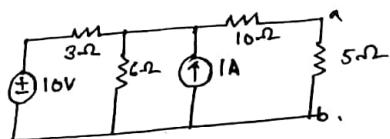3. Find the current in the 5Ω resistor for the circuit shown.



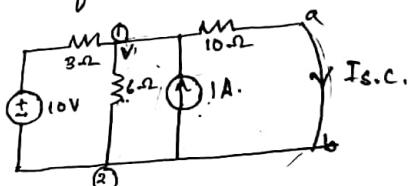Sol. Let us first remove the 5Ω resistor and short the a-b terminals.



Assuming the voltage to be +ve at node 1, nodal analysis gives.

$$\frac{V-10}{3} + \frac{V}{6} - 1 + \frac{V}{10} = 0.$$

$$\text{or, } 0.33V + 0.17V + 0.1V = 4.83.$$


$$\text{or, } V = 7.22V.$$

Applying KVL at the right most loop (i.e. a-b-2),


$$V = 10 \times I_{s.c.}$$

$$\text{or, } I_{s.c.} = 0.722 \text{ A} (= I_N).$$


find Norton's
impedance is
deactivated.

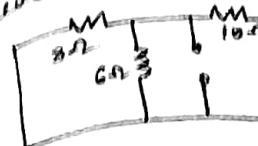


find the Norton's

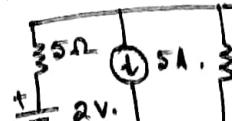


↓ show

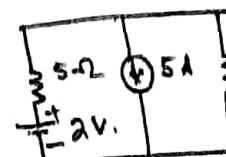

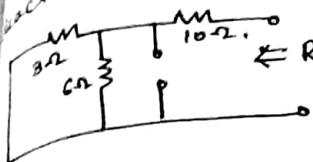find Norton's Equivalent resistance is removed and all the constant sources are deactivated.



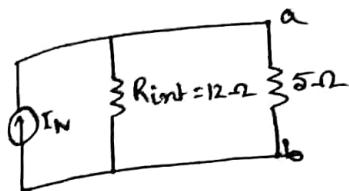
$$R_{int} = \frac{3 \times 6}{3 + 6} + 10 = 12 \Omega.$$




Norton's Equivalent Circuit being shown in fig, Current through 5Ω resistor is

$$I_{5\Omega} = I_N \cdot \frac{R_{int}}{R_{int} + 5} = 0.722 \times \frac{12}{12+5} = 0.5096 A \approx 509.6 \text{ mA.}$$

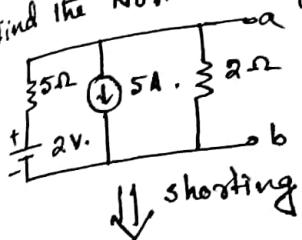
find the Norton's equivalent circuit across a-b for the w/o shorun.




↓↓ shorting terminal a-b.

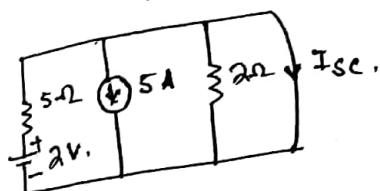


2Ω -resistor
bypassed

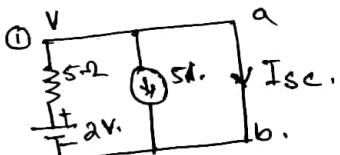
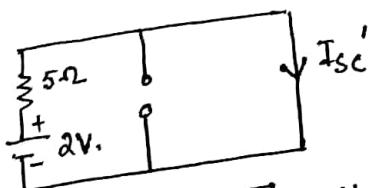
$$\text{Taking first } 2V \text{ source}; \\ 2 = 5 \times I_{sc}^1 \Rightarrow I_{sc}^1 = 0.4 A.$$


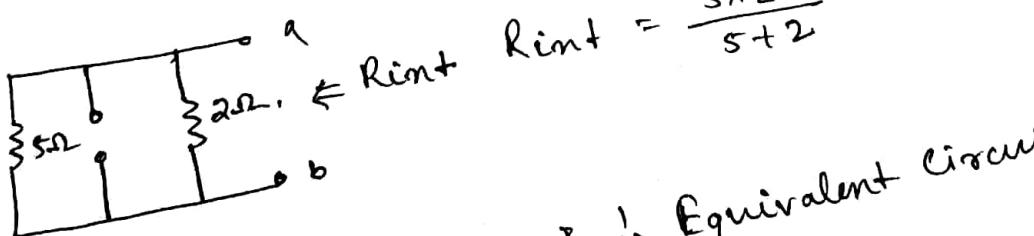
$$\text{Taking } 5A \text{ source only, } I_{sc}^{II} = -5 A. \\ \text{Using principle of superposition, } I_{sc} = I_{sc}^I + I_{sc}^{II} = -4.6 A.$$



Norton's Equivalent circuit.



thus we observe that the voltage across the capacitor being constant, current through it is zero. This means that the capacitor, on application of dc voltage and with no initial charge first acts as short circuit but as soon as the full charge is attained, the capacitor behaves as open circuit. It can store finite amount of energy, even if the ct. thru it is zero. ③

Inductance:

Inductance is the property of a material by virtue of which it opposes any change of magnitude or direction of electric current passing thru the conductor.

Any change of field induces a voltage (V_L) across the coil, given by (Lenz's law)

$$V_L = -L \frac{di}{dt}$$

i is the current through the inductor in ampere.

Thus, in a pure inductive circuit with applied voltage V , we can write. $V + V_L = 0$

$$\text{or, } V = -V_L = L \frac{di}{dt}$$

The voltage across the inductor would be zero if the current through it remains const. This means that an inductor behaves as a short circuited coil in steady state, when direct steady ct. flows thru. it. However for any small change in current strength or change in direction, inductance will appear. It may also be observed that for a minute change in current within zero time it gives an infinite voltage across the inductor which is physically not at all feasible. Thus in an inductor current cannot change abruptly.

Thus it behaves as open circuit just after switching across d.c. voltage but as short circuit at steady state.

$$\text{Power absorbed } P = V \times i = Li \frac{di}{dt} \text{ watt.}$$

$$\text{Energy stored } W = \int_0^t P dt = \int_0^t Li \frac{di}{dt} dt = \frac{1}{2} L i^2.$$

So it is evident that inductor can store finite amount of energy, even the voltage across it may be nil. A pure inductor does not dissipate energy, but only stores it.

Time Domain

$$R: v = Ri(+)$$

L: Initial current is $i(0^+)$, clockwise circuit being $i(+)$;
 $v(+)=L\frac{di(+)}{dt}$

current in the inductor
is given by
 $i(+)=\frac{1}{L}\int_0^+ v(+)\,dt + i(0^+)$

C: Initial voltage is V_0 , with
+ve polarity at the side
of the capacitor that
opposes charging ct.
 $i(+)$ thru-
 $v(+)=V_0 + \frac{1}{C}\int_0^+ i(+)\,dt.$

when assist charging ct.
 $i(+)$
 $v(+)=-V_0 + \frac{1}{C}\int_0^+ i(+)\,dt.$

Current in the capacitor
is given by
 $i(+)=C\frac{dv(+)}{dt}$

S-Domain

$$v(s) = R I(s).$$

$$v(s) = [sLI(s) - Li(0^+)]$$

$$\begin{aligned} I(s) &= \frac{1}{L} \cdot \frac{v(s)}{s} + \frac{i(0^+)}{s} \\ &= I_L(s) + I_o(s), \\ \frac{i(0^+)}{s} &= I_o(s). \end{aligned}$$

$$I_L(s) = \frac{v(s)}{sL}$$


$$v(s) = \frac{V_0}{s} + \frac{1}{C} \frac{I(s)}{s} = \frac{V_0}{s} + \frac{I(s)}{Cs}$$

$$v(s) = -\frac{V_0}{s} + \frac{I(s)}{Cs}$$

$$I(s) = C[v(s)s - V(0^+)]$$

$$\left[\frac{v(s)}{1/Cs} = v(s)Cs \right]$$

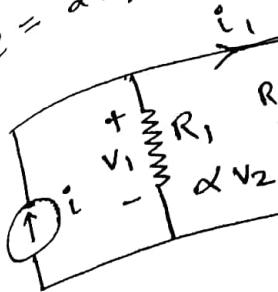using the principle
voltage $v_2(+)$
 $C = 2F, \beta = 2$



Set $v(+)$

Let $v_1(s)$
equations are
 $I(s)$

$v_1(s)$
 v_2


Elimination
values,

Set $i(+)$


The

Nabanita Chatterjee - (EE Faculty)

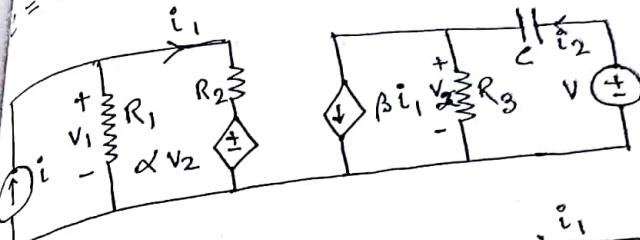Using the principle of superposition, calculate V_o .
 Using $V_2(+)$ in fig. Assume $R_1 = R_2 = 1\Omega$, $R_3 = 0.5\Omega$,
 $C = 2F$, $\beta = 2$, $\alpha = 1$, $i(+)$ = $\sin t$, $v(+)$ = t .



Set $v(+)$ = 0.

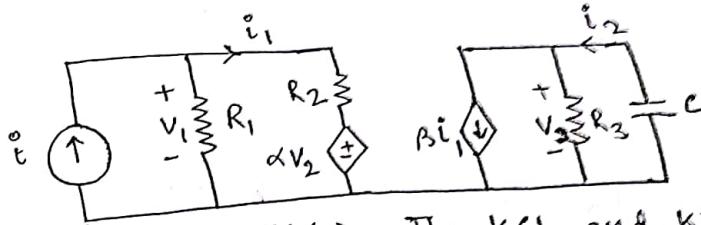

$\frac{I(s)}{s} = \frac{V_o}{s} + \frac{I(s)}{Cs}$ Let $V_1(s) = t V_1(+)$, $I(s) = t i(+)$. The KCL and KVL equations are,

$$I(s) = \frac{V_1(s)}{R_1} + I_1(s)$$

$$V_1(s) = \alpha V_2'(s) + R_2 I_1(s)$$


$$V_2'(s) = -\beta I_1(s) \frac{1}{1/R_3 + sC}$$

Eliminating $I_1(s)$, $V_1(s)$ and substituting parameter values,

$$V_2'(+) = t^{-1} V_2'(s) = t^{-1} - \frac{1}{2} \left(-\frac{1}{s+0.5} \right) \left(\frac{1}{s^2+1} \right)$$

$$= -\frac{2}{5} e^{-0.5t} - \frac{1}{\sqrt{5}} \sin(t - 63.5^\circ)$$

Set $i(+)$ = 0

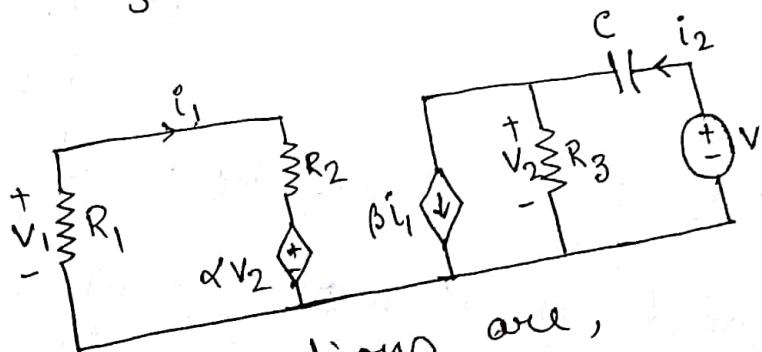

The KCL and KVL equations are,

$$I_2(s) + V_2''(s)$$

$$V(s) = \frac{sC}{sC}$$

$$V_2''(s) = I_2(s) - \beta I_1(s)$$

$$I_1(s) = \frac{-\alpha V_2''(s)}{R_1 + R_2}$$


Eliminating $I_1(s)$ and $I_2(s)$ and substituting parameter values,

$$V_2''(+) = \mathcal{L}^{-1} V_2''(s) = t^{-1} \left(\frac{s}{s+2} \right) \frac{1}{s^3} = \left(\frac{1}{4} t^{\frac{3}{2}} + \frac{t}{2} - \frac{1}{4} \right)$$


Then the total solution.

$$v_2(+) = v_2'(+) + v_2''(+) = \left[-\frac{2}{5} e^{-t/2} + \frac{1}{4} e^{-2t} - \frac{1}{4} - \frac{1}{\sqrt{5}} \sin(t - 63.5^\circ) + \frac{t}{2} \right] u(t)$$

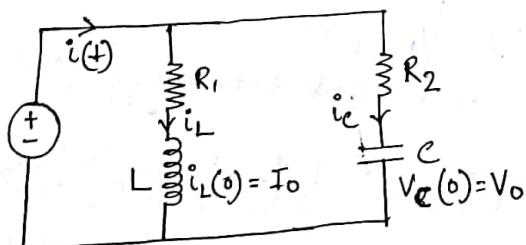2. Calculate the driving point current for the network by converting all initial conditions into equivalent sources and applying the superposition theorem. Assume $R_1 = 3\Omega$, $R_2 = 1\Omega$, $L = 2H$, $C = 0.5F$, $v_C(0) = V_0 = -3V$, $i_L(0) = I_0 = 1A$, $v(+)$ = $v(+)$, a unit step.



Circuit with initial conditions.

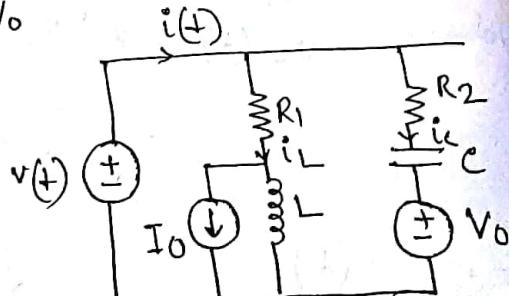

- i) Set $I_0 = 0$, $V_0 = 0$ and let $i(+) = i'(+)$.

Equivalent circuit with current source eliminated and $V_0 = 0$

